

Basic Electrical Engineering

UNIT-I

D.C Circuits

Concept of Charge

The charge is a particle, which experiences a force when it is placed in a electric (or) magnetic fields. It is denoted as 'Q' or 'q'.

The unit of charge is "Coloumb (C)".

1 coloumb = charge on 6.24×10^{18} electrons

i.e $1 e^- = -1.602 \times 10^{-19}$ coloumb.

Electric Current (I)

The electric current can be defined as "rate of flow of charge (i.e electrons) in an electric circuit" (or) "in any conductive or semiconductive mediums.

$$\text{i.e } i = \frac{dq}{dt} \Rightarrow I = \frac{Q}{t}$$

where I = Average current in circuit

Q = Total charge transferred in circuit

t = time taken for charge.

Units for current is Amperes (Amp) (or) (Coloumb/sec)

1-Ampere :- "When 1-coloumb of charge is transferred in a circuit in 1-second, then 1-Ampere current is flowing in that circuit.

Electric Voltage (or) Electric Potential (V)

Potential difference (or) Voltage

The Voltage (V) is defined as "an electromotive force which causes the flow of charge (i.e. electrons) in an electric circuit."

(or)

The ability of charge particle to do work in an electric circuit is called "electric potential."

$$\text{i.e. } V = \frac{dW}{dq} \Rightarrow V = \frac{W}{Q}$$

where V = Total voltage across two terminals

Q = Charge in electric circuit

W = Work done in electric circuit


Units for voltage is Volts (V) (or) (Joules/Coulomb)

1 Volt: When 1-coulomb of charge is transferred between two points with 1-joule of work, then 1-volt potential is exist between the two points.

Ex:-



Inside piece of conductor

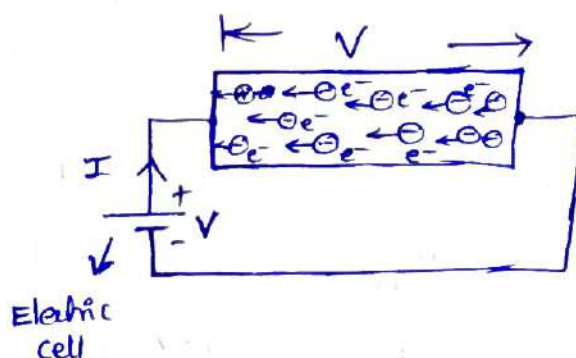

Electric Power or Power (P)

The electric Power can be defined as "the rate of electric workdone in an electric circuit is called as "Power"

(or) "the rate of flow of electrical energy in electric circuit.

$$\text{i.e } P = \frac{dW}{dt} \Rightarrow P = \frac{dW}{dq} \times \frac{dq}{dt} \Rightarrow \boxed{P = VI}$$

i.e Power is Product of Voltage & Current

Units for Power is Watts (W)

Electrical Energy (E)

An Electrical energy is the total amount of electrical work done in an electric circuit

$$\text{i.e } E = P \times \text{time} \Rightarrow \boxed{E = VIt} \text{ Joules}$$


Units for Electrical Energy is Watt-hr (or kWh)

Electric Circuit

An electric circuit is a closed conducting path through which an electric current flows


(or)

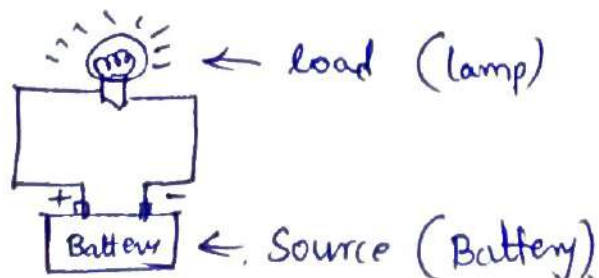A closed path which consists of supply source & load with conductors is called "Electric circuit"



Electrical Network:- Network is a combination of circuit & which consist of more no. of sources & loads, and it may be closed or open circuit (i.e any arrangement)

Ex:-

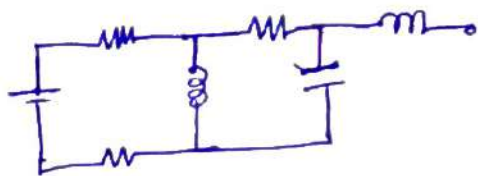

Types of Circuit Elements:-

Active Elements:- An elements which are capable of supplying (or) delivering the power is called "Active elements"

Ex:- Voltage Source
Current Source


Passive Elements:- An elements which are capable of receiving (or) utilizing the power is called "Passive elements".

Ex:- Resistor, Inductor, Capacitor. etc

Linear Elements:-

The $V-I$ characteristics of an elements is at all times a straight line & passing through the origin, thus elements are called "Linear elements"


Example :- R, L, C

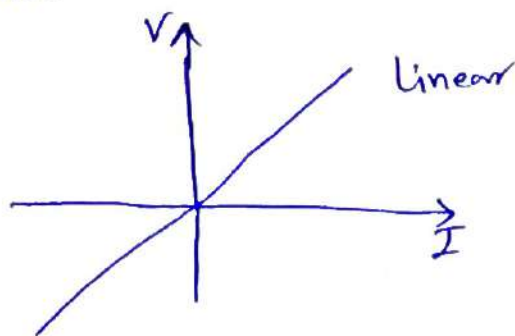

Non-Linear Elements:-

The V-I characteristics of an element is at all times not a straight line and not passing through a origin, thus elements are called "Non-linear elements"

Ex:- Transistor, Diode

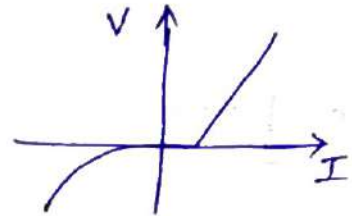

Bilateral Elements:-

Those elements characteristics & behaviour are independent of direction of current, thus elements are called "Bilateral Elements".

Ex:- Resistor, Inductor, Capacitor, Transformer

Unilateral Elements:-

Those elements characteristics & behaviour are dependent on direction of current, thus elements are called unilateral Elements.

Ex:- Diode, Triode.

Lumped Elements:-

The elements which are possible to separate from the network physically, these elements are called Lumped elements

Ex:- R, L, C & transformer, diode,

Distributed Elements:- The elements which are not possible to separate from the network physically,

Ex:- Transmission line R-L-C parameters.


Ohm's Law

Statement:- Ohm's Law states that "the current passing through a conductor is directly proportional to the applied voltage across the conductor, at constant temperature 'T'.

i.e. $V \propto I$ (or) $I \propto V$

$$V = IR$$
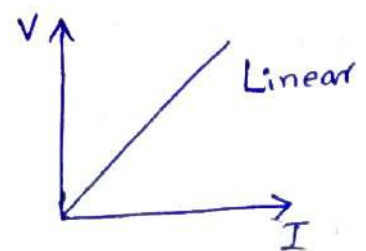
$$I = \frac{V}{R} \quad \& \quad R = \frac{V}{I}$$



V-I - characteristics

Where 'R' is resistance of conductor. (units Ω).

Limitations of Ohm's Law:-

- ①. It is not applicable to temperature varying devices
- ②. It is not applicable to non-linear devices
- ③. It is not applicable to semiconductive materials.

Electrical Circuit Elements

In Electrical ~~field~~ field we have 3-types of electrical circuit elements, as

- ① Resistor (R)
- ② Inductor (L)
- ③ Capacitor (C)

Resistance (R) :- "The property of material which opposes (or) restricts the flow of electrons through material is called "Resistance". The element having this property is called "Resistor (R)"

→ It's symbol is 

→ Units are "Ohm" is " Ω "

→ Power absorbed by resistor $P = VI \Rightarrow \begin{cases} P = (IR)I = I^2R \\ = V(\frac{V}{R}) = \frac{V^2}{R} \end{cases}$

→ Energy lost in the resistor in a time 't'

$$W = \int_0^t P dt = P \cdot t = I^2 R t \text{ or } \frac{V^2}{R} t.$$

→ Reciprocal of the resistance is called "Conductance" (G)

i.e. $G = \frac{1}{R} \rightarrow \text{unit "mho" } (\Omega^{-1})$

→ 1Ω is defined as "when 1V voltage is applied across a resistor, then 1A current flows, it having resistance is " 1Ω ".

Factors affecting resistance:-

- ① Length of material (l)
- ② Cross-sectional area (a)
- ③ Type of material (or) Nature of material (ρ)
- ④ Temperature (T).

i.e $R \propto \frac{l}{a} \Rightarrow \boxed{R = \frac{\rho l}{a}} \Omega$

where l = length of material

a = area of cross-sectional

ρ = Resistivity (or) Specific Resistance

Resistivity (or) Specific Resistance:- (ρ)

It is a fundamental property (or) natural property of material which opposes the flow of current is called resistivity (ρ)

i.e $\boxed{\rho = \frac{R a}{l}} \quad \boxed{\text{units are } "\Omega\text{-m}"}$

Conductance (G) : The property of material which allows the flow of electrons in a conductor is called as "conductance"

i.e $G = \frac{1}{R} \Rightarrow \frac{a}{\rho l}$ — i.e reciprocal of 'R' is called "G".

$\boxed{\text{Units are "Siemens"}}$

→ The reciprocal of resistivity is called "conductivity (σ)".

$\boxed{\sigma = \frac{1}{\rho}}$

units $(\Omega\text{-m})^{-1}$

Inductance (L) : Inductance is the property of a material ~~which~~ (or) element which stores the electrical energy in the form of magnetic field.

(or)
"the property of a material which opposes ~~the~~ any change of magnitude (or) direction of electric current passing through the material (or) element."

→ It's Symbol is 

→ Units are "Henry (H)"

→ The voltage across the ^{inductor is} ~~is~~ directly proportional to the rate of change of current

$$V(t) \propto \frac{di(t)}{dt}$$

i.e.
$$V_L = L \frac{dI}{dt}$$
 voltage across inductor

→ The current flowing through the inductor is

$$I_L = \frac{1}{L} \int_0^t V dt + I_0$$

→ Power absorbed by the inductor is

$$P = V \times i \Rightarrow LI \cdot \frac{di}{dt} \text{ watts.}$$

Energy stored in Inductor:-

The total energy in a inductor is

$$W_L = \int P_L(t) dt$$

$$= \int L \cdot i \cdot \frac{di}{dt} \cdot dt$$

$$= \int L \cdot \frac{i^2}{2} di \Rightarrow W_L = L \cdot \frac{i^2}{2} \Rightarrow \boxed{W_L = \frac{1}{2} L i^2} \text{ Jouly}$$


Capacitance (C)

Capacitance is the property of a element (or) material which stores electrical energy in the form of electric field.

(or)

the property of element which opposes sudden changes in magnitude of applied voltage across the element.

→ It's Symbol is

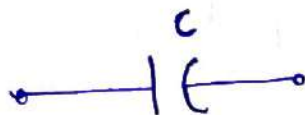

→ Units are "Farads (F)"

→ The amount of charge (q) that can be stored in a capacitor of capacitance 'C' depends on applied voltage (V)

$$\text{i.e. } C = \frac{q}{V}$$

$$\therefore i = \frac{dq}{dt}$$

$$\text{i.e. } \boxed{i_c = C \frac{dV}{dt}}$$

Current flowing capacitor

→ Voltage across capacitor

$$\boxed{V_c = \frac{1}{C} \int i dt + V_0}$$

(6)

→ Power absorbed by capacitor

$$P = Vi = v c \frac{dv}{dt}$$

→ Energy stored in capacitor:-

The total energy in a capacitor is

$$W_c = \int P_c(t) dt$$

$$= \int v c \frac{dv}{dt} \cdot dt$$

$$= c \cdot \frac{v^2}{2} \Rightarrow \boxed{W_c = \frac{1}{2} c v^2} \text{ Joules.}$$

Problems:-

Q:- Find the energy dissipation and stored by the passive elements R & L, C.

- (i) A resistance 5Ω carries current of 2A ~~at~~ ^{for} ~~3~~ 3 hours
 (ii) A 10 H inductor carries a current 5A ~~at~~
 (iii) 30 ~~000~~ F capacitor having applied voltage 20V

(Ans:- $E_R = 60 \text{ Wh}$
 $E_L = 125 \text{ J}$
 $E_C = 6000 \text{ J}$)

Q Find the values of R, L & C

- (a) A resistance carries 2A at 500V
 (b) A inductor carries 2A and 20J of energy is stored
 (c) A capacitor with 500V across it and 20J is stored energy

(Ans:- $R = 250\Omega$
 $L = 10 \text{ H}$
 $C = 1600\mu\text{F}$)

Voltage and Current Sources

These are classified as two types

① Independent Sources


② Dependent Sources.

① Independent Sources : The values of energy sources does not depend on other voltages (or) currents in the network, thus sources are called "Independent Sources".


(i) Independent Voltage Source :-

The energy source which maintains constant voltage at its terminals irrespective of the current delivered to the external circuit, is called "Independent Ideal Voltage Source".

→ Symbol is

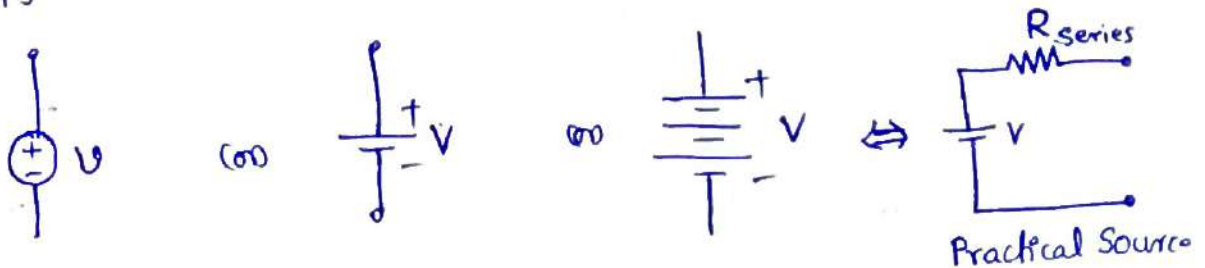

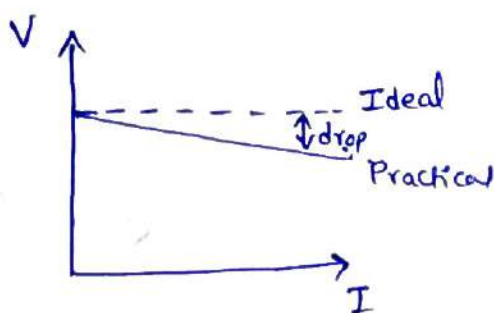→ Practically it has a small internal resistance in series, due to this some amount of voltage drop is exist as shown below



* Internal resistance of an ideal voltage source is $R=0$ i.e. $V_p = V_{o/p}$

(ii) Independent Current Source


The source which delivers a current of constant magnitude at its terminals irrespective of applied voltage across its terminals is called "Independent Ideal Current Source".

→ Symbol is




Ideal Source

&

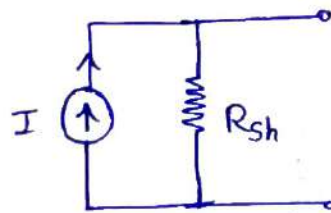

Practical Source

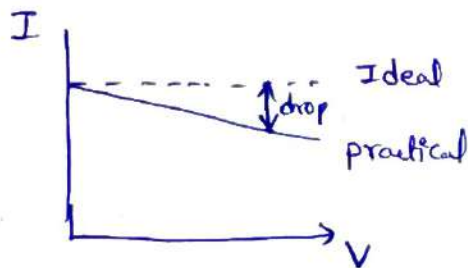→ But practically it has high internal resistance connected parallel with it, due to this some amount of drop will exist as shown below.



* Internal resistance of an ideal current source i.e. $R = \infty$ i.e. infinite

(2) Dependent Sources:-


The values of energy sources are depends on other voltages (or) currents in the network, thus sources are called "Dependent Sources".

These are classified as 4-types

- ① voltage ~~Dependent~~ dependent Voltage Source (VDVS)
- ② Voltage Dependent Current source (VDCS)
- ③ Current Dependent Voltage source (CDVS)
- ④ Current Dependent Current source (CDCS)


①. Voltage Dependent voltage Source (VDVS)

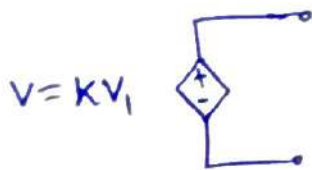The value of this voltage source depends on function of voltages in elsewhere in the same circuit.



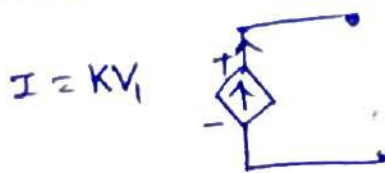
(ii) Voltage Dependent Current source (VDCS)

The value of this current source depends on function of ~~voltages~~ ~~currents~~ in elsewhere in the same circuit



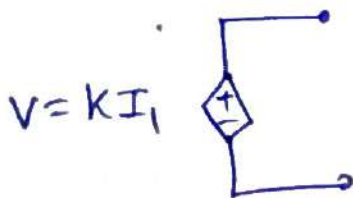(iii) Current Dependent voltage Source (CDVS)

The value of this voltage source depends on function of currents in somewhere in the same circuit



(iv) Current dependent Current source (CDCS)

The value of this current source depends on the function of current in somewhere in the same circuit




Series & Parallel connections of R, L & C electrical elements

① Resistors connected in Series

In a series circuit, all the components are connected such that there is only one closed path and same current flows through all the components. As shown in below figure

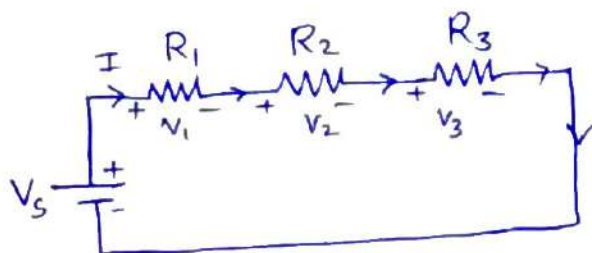consider 3-Resistors
 R_1 , R_2 & R_3 are connected in series with a voltage source V_s & causes the current I .



The total (or) Equivalent resistance of circuit

is

$$R_{eq} = R_1 + R_2 + R_3$$

Note :- ① In series circuit Current is Same $I_s = I$

② In series circuit Voltage is divided

i.e $V_s = V_1 + V_2 + V_3$

⇒ Application of series connection is to increase the resistance & to limit the current flow.

⇒ Resistances, Voltages & powers are additive in series connection.


⇒ Different current rating devices unable to connect in series.

② Parallel connection of Resistors

In parallel circuit "all the components in that circuit are connected in a manner that there are more than one path or branches current can flow.

As shown below

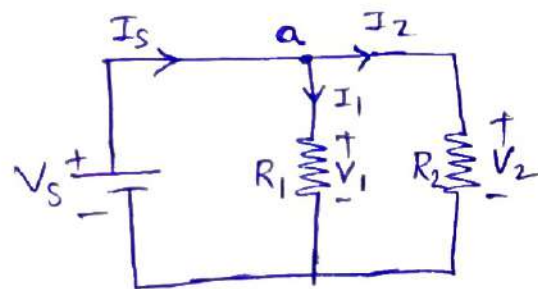Consider a circuit having two resistors R_1 & R_2 in parallel across a source V_S & point 'a' current is



$$I = I_1 + I_2$$

The equivalent Resistance is

$$\boxed{\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}}$$

$$\text{or } \boxed{R_{eq} = \frac{R_1 R_2}{R_1 + R_2}}$$

Note :- ① Parallel circuit Voltage is Same $V_S = V_1 = V_2$

② Current is divided i.e. $I_S = I_1 + I_2$

Advantages :-

① If there is a discontinuity or break in any one branch, the current will still flow in the other branch.

② The power & current rating can be distributed to the electrical appliances is same.


③ These are used in all household & industrial wiring.

③ Inductors in Series




$$\Rightarrow L_{eq} = L_1 + L_2$$

④ Inductors in parallel

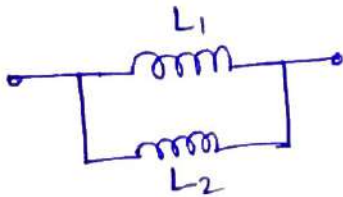


$$\Rightarrow L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$$

⑤ Capacitors in series

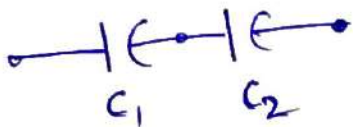

$$\Rightarrow \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} \Rightarrow C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$


⑥ Capacitors in Parallel

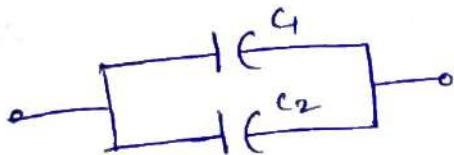

$$\Rightarrow C_{eq} = C_1 + C_2$$

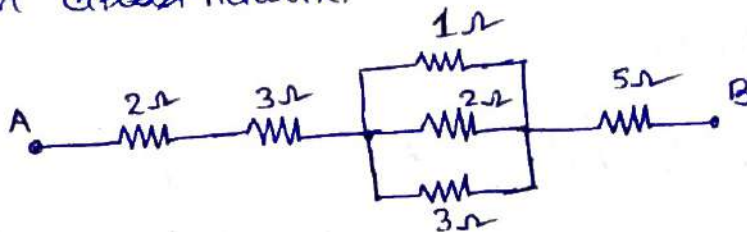
Problem :-

- ① Find the total Resistance between the terminal A & B for given circuit network.




Solution:- In given circuit 2Ω & 3Ω resistors in series

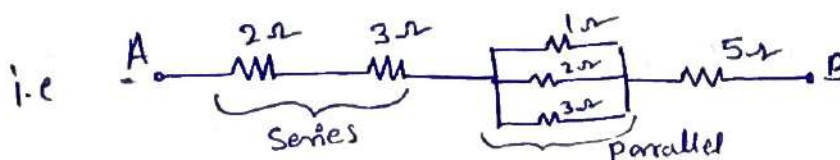& $1\Omega, 2\Omega, 3\Omega$ are in parallel



The circuit modified as

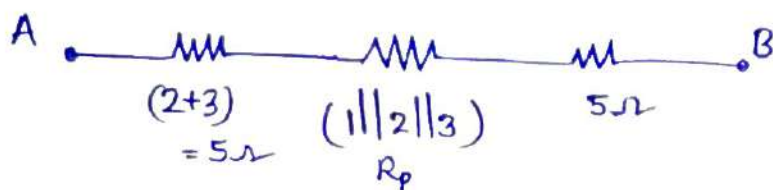


$$R_p = \frac{1 \times 2 \times 3}{2 + 6 + 3}$$

$$= \frac{6}{11}$$

$$\therefore R_{eq} = \frac{R_1 R_2 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

then

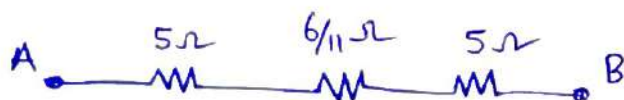

Now

$$\text{Total Resistance } R_{AB} = 5 + \frac{6}{11} + 5 = 5 + 0.545 + 5$$

$$= 10.545$$

$$R_{AB} = 10.545 \Omega$$

- ② Determine the voltage if the total power absorbed by the resistors is 100 Watts, thus resistor are 2Ω , 3Ω , 4Ω & 5Ω respectively are connected in parallel.

Solution:-

Given data: $R_1 = 2\Omega$, $R_2 = 3\Omega$, $R_3 = 4\Omega$, $R_4 = 5\Omega$ & $P = 100 \text{ Watts}$

Then in parallel R_T is

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \Rightarrow \frac{1}{2} + \frac{1}{3} + \frac{1}{4} + \frac{1}{5}$$


$$= \frac{30 + 20 + 15 + 12}{60} = \frac{77}{60} \Rightarrow R_T$$

The total power absorbed $P = \frac{V^2}{R_T} = 100 \text{ W}$

$$V^2 = 100 \times R_T \Rightarrow 100 \times \frac{77}{60} = V_s = 8.827 \text{ Volts}$$

Basic Definitions

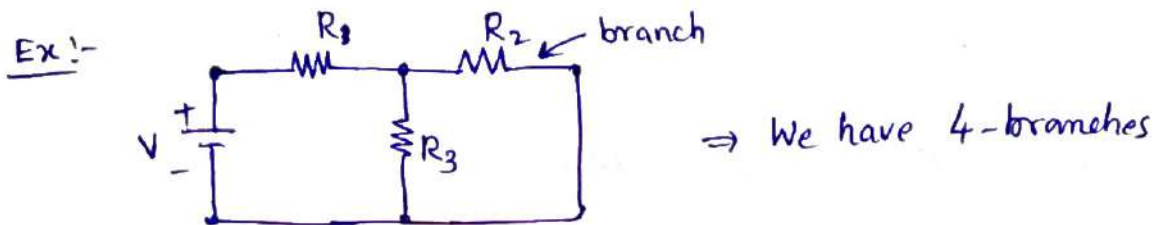
Branch :- "A part of a network which is connected between two nodes, usually called as 'branch'".




Node :- "A point at which two or more circuit elements are joined together is called 'node'".



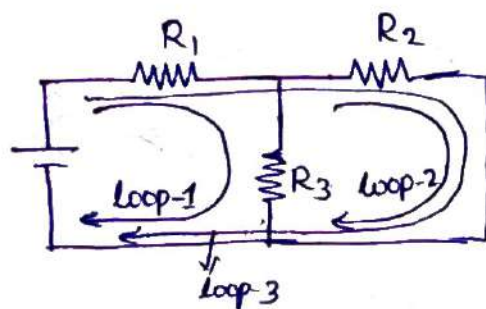Mesh (or) Loop :- "A closed path which starts and ending at same node and which is not passing any node (or) branch twice is called mesh (or) loop".



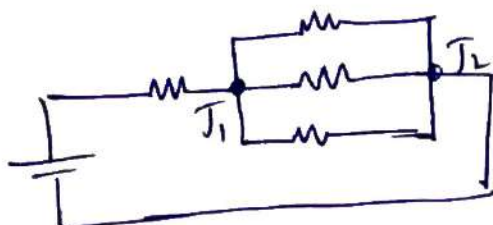Junction Point :- A point of a network at which three or more no. of circuit elements are joined together



Kirchhoff's Laws

Kirchhoff's Laws are classified into two types

① Kirchhoff Current Law (KCL)

② Kirchhoff Voltage Law (KVL)

Kirchhoff Current Law (KCL)

Statement :- KCL states that algebraic sum of currents at any node is equal to "zero". i.e


the total current entering a node is equal to the total current leaving that node.

i.e $\boxed{\sum_{\text{at node}} I = 0}$

or $\boxed{\sum I_{\text{ent}} = \sum I_{\text{leav}}}$

Explanation :-

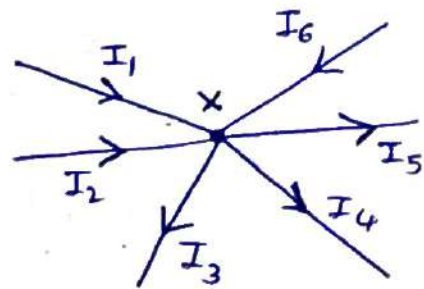consider a node 'x' is connected by a 6-branches carrying a currents I_1, I_2, I_3, I_4, I_5 & I_6 as shown in fig.



Let the currents entering into the node are positive currents & leaving currents are negative currents as

I_1, I_2, I_6 are positive

& I_3, I_4, I_5 are negative

Then, According to KCL

$$\sum I = 0 \quad \text{i.e.} \quad I_1 + I_2 - I_3 - I_4 - I_5 + I_6 = 0$$

$$\text{(or)} \quad I_1 + I_2 + I_6 = I_3 + I_4 + I_5$$

i.e. from KCL

Total current entering into node = Total current leaving from that node.

→ It is useful for Nodal analysis

Kirchhoff Voltage Law (KVL)


Statement :- KVL states that algebraic sum of the voltages around the closed loop (or) circuit is equal to zero

i.e. $\boxed{\sum_{\text{In loop}} V = 0}$

i.e. the algebraic sum of the emf's (or) voltages of sources in loop is equal to sum of the voltage drop across the circuit elements of in that loop

i.e. $\boxed{\sum_{\text{loop}} V_s = \sum_{\text{loop}} (IR)_{\text{drop}}}$

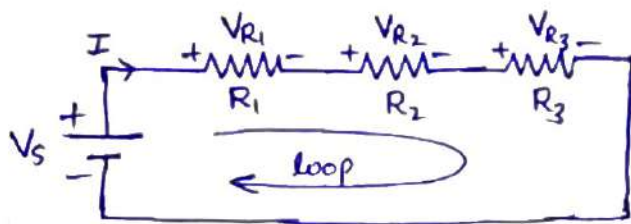Explanation:- consider a circuit which is having resistors R_1 , R_2 & R_3 & supply source V_s as shown below



According to KVL

$$V_s - V_{R_1} - V_{R_2} - V_{R_3} = 0$$

$$V_s = V_{R_1} + V_{R_2} + V_{R_3}$$

$$= IR_1 + IR_2 + IR_3$$

$$V_s = I(R_1 + R_2 + R_3) \Rightarrow I = \frac{V_s}{R_1 + R_2 + R_3}$$

→ Indicate the sign conventions for elements by the direction of currents


→ It is useful for mesh analysis.

Steps for applying Kirchhoff Laws:-


- step ① Draw the circuit diagram from given information
- ② Insert the all values of sources with appropriated polarities and all resistance values
- ③ By using KCL mark the all branch currents with some assumed directions at the nodes.
- ④ Mark the all the polarities of voltage drops or rises & drops
- ⑤ Apply KVL for different closed loops
- ⑥ Solve the equations by based on solution

Problems:-

P1 Determine the current in all resistors in the by using KCL, for a given circuit below

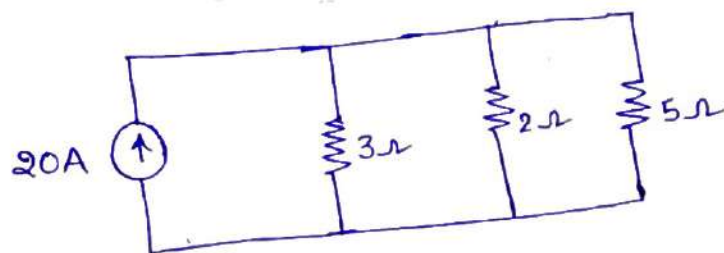Solution:-

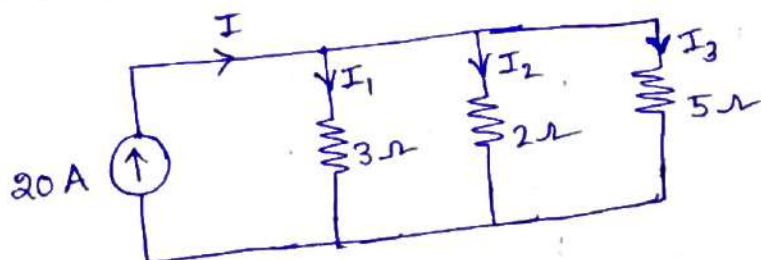Let the total current I , & respective branch currents I_1, I_2, I_3 as shown circuit & let the voltage 'V'



According to KCL

$$I = I_1 + I_2 + I_3$$

$$20 = \frac{V}{3} + \frac{V}{2} + \frac{V}{5}$$

$$20 = V \left[\frac{1}{3} + \frac{1}{2} + \frac{1}{5} \right]$$

$$20 = V \left[\frac{10 + 15 + 6}{30} \right] \Rightarrow V = \frac{20 \times 30}{31} \Rightarrow \boxed{V = 19.35 \text{ V}}$$

$\therefore$ By the Ohm's law

$$\therefore I = \frac{V}{R}$$

$$\therefore I_1 = \frac{V}{3}$$

$$\therefore I_2 = \frac{V}{2}$$

$$\therefore I_3 = \frac{V}{5}$$


Now branch currents

$$\text{Current in } 3\Omega \text{ Resistor } I_{3\Omega} = I_1 = \frac{V}{3} = \frac{19.35}{3} \Rightarrow \boxed{I_1 = 6.45 \text{ A}}$$

$$\text{Current in } 2\Omega \text{ Resistor } I_{2\Omega} = I_2 = \frac{V}{2} = \frac{19.35}{2} = \boxed{I_2 = 9.67 \text{ A}}$$

$$\text{Current in } 5\Omega \text{ Resistor } I_{5\Omega} = I_3 = \frac{V}{5} = \frac{19.35}{5} = \boxed{I_3 = 3.87 \text{ A}}$$

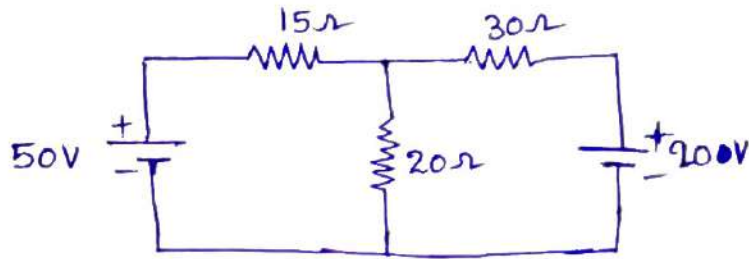
P2 Apply Kirchhoff's laws to the given circuit



Determine the currents in all branches.

Solution:-

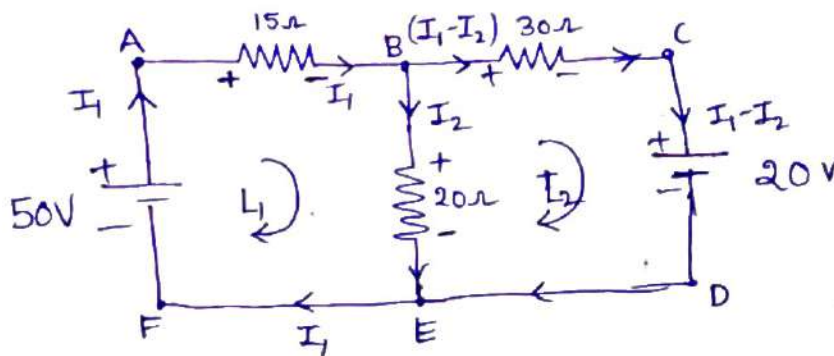Steps ① & ② Draw the circuit diagram with the values & polarities & branch currents by 50V source as reference, by KCL



→ Apply KVL for different loops L_1 & L_2

Loop 1 : ABEFA

$$50 - (I_1 \times 15) - (I_2 \times 20) = 0$$

$$15I_1 + 20I_2 = 50 \quad \text{--- (1)}$$

Loop 2 :- BCDEB

$$- 30 \times (I_1 - I_2) - 20 + (20 \times I_2) = 0$$

$$- 30I_1 + 30I_2 + 20I_2 = 20$$

$$- 30I_1 + 50I_2 = 20 \quad \text{--- (2)}$$

By solving the equations ① & ②

Multiply eq ① $\times 2$ ~~2~~ ~~eq 1~~

(or) use the
casio

then

$$\begin{array}{r} 30I_1 + 40I_2 = 100 \\ -30I_1 + 50I_2 = 20 \\ \hline 90I_2 = 120 \Rightarrow I_2 = \frac{120}{90} \Rightarrow I_2 = 1.33 \text{ Amp} \end{array}$$

Substitute I_2 in eq ① or ②.

$$15I_1 + (20 \times 1.33) = 50$$

$$I_1 = \frac{(50 - 26.6)}{15} \Rightarrow I_1 = 1.56 \text{ Amp}$$

Now branch current

Current in 15Ω Resistor

$$I_{15\Omega} = I_1 = 1.56 \text{ Amp}$$


Current in 20Ω Resistor

$$I_{20\Omega} = I_2 = 1.33 \text{ Amp}$$

Current in 30Ω Resistor


$$I_{30\Omega} = (I_1 - I_2) = 0.23 \text{ Amp}$$

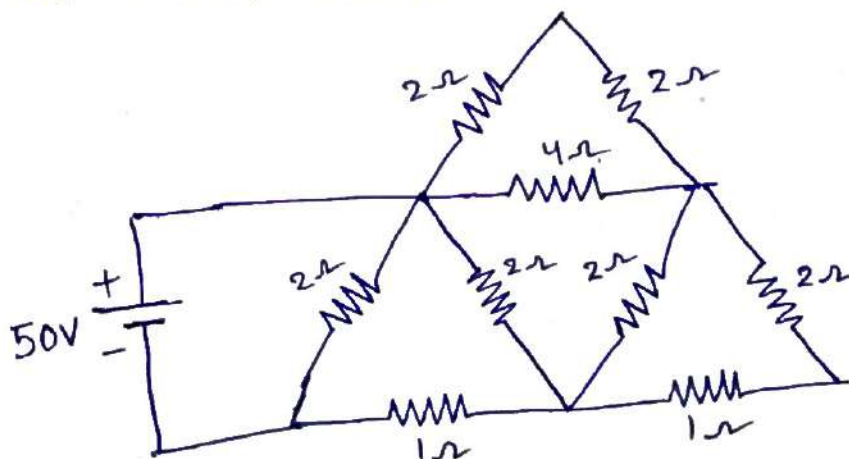P3 :- Determine the current delivered by the source in the circuit shown in below.



$$\text{Ans: } I = 47.41$$

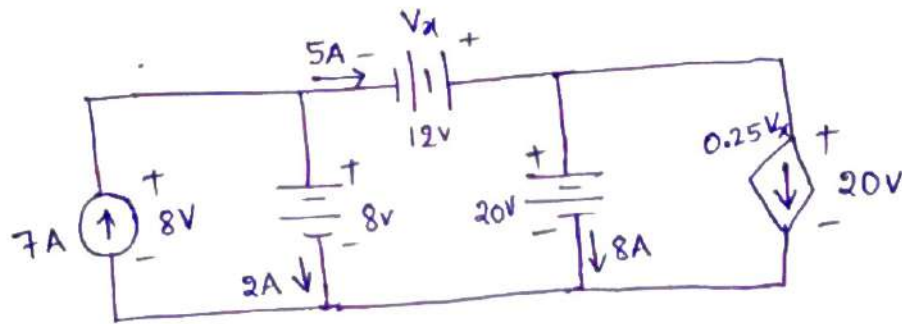Q: Calculate the power absorbed by each component in the circuit shown in figure.



Solution:- In a given circuit we have 5-components a)
 3- voltage sources
 1- Current source & 1- voltage dependent current source.

Now Power absorbed by

7A current source is $P_{7A} = V \times I = 7 \times 8 \Rightarrow \boxed{P_{7A} = 56W}$


8V voltage source is $P_{8V} = 8 \times (-2) = -16 \Rightarrow \boxed{P_{8V} = -16W}$

12V voltage source is $P_{12V} = 5 \times 12 = 60 \Rightarrow \boxed{P_{12} = 60W}$

20V voltage source is $P_{20V} = 20 \times (-8) = -160 \Rightarrow \boxed{P_{20} = -160W}$

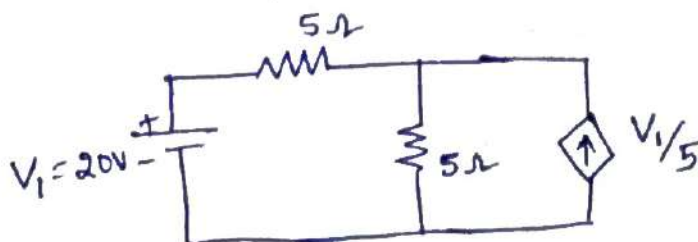0.25V_x VDCS is $P = (0.25 \times 12) \times (20) = 60 \Rightarrow \boxed{P_{VDCS} = 60W}$

Q:- Find the power supplied by dependent source.



Ans: $\boxed{80W}$

Analysis of simple DC-circuits

Analysis of DC-circuits can be done by Network Reduction techniques as


- Source transformation
- Current division rule
- Voltage division rule
- Nodal Analysis
- Mesh Analysis
- Star-Delta or Delt-Star transformation:-

Source Transformation:-

Source transformation is technique for "reducing of complexity of network by replacing voltage source by current source (or) current source by voltage source."

Practically we know that voltage source has a series resistance and current source has a parallel (shunt) resistance.

Let the Voltage & current sources as

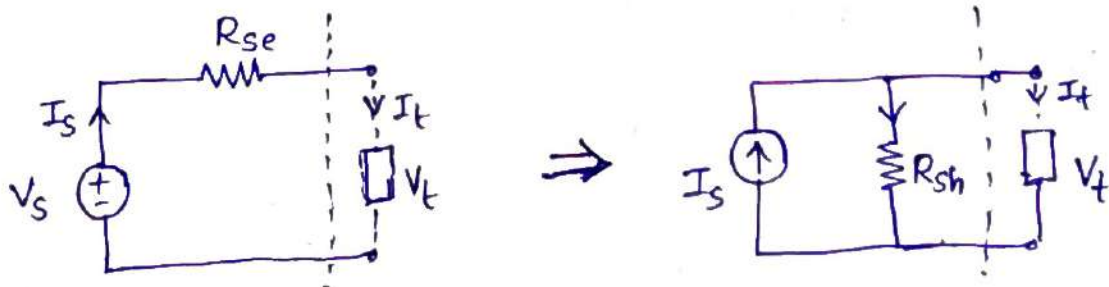

When $R_{se} = R_{sh}$, then Source Transformation is possible

$$V_t = V_s - I_s R_{se} \quad (\because I_s = I_t)$$

$$I_t = \frac{V_s - V_t}{R_{se}}$$

$$I_t = \frac{V_s}{R_{se}} - \frac{V_t}{R_{se}} \Rightarrow I_t = I_s - \frac{V_t}{R_{se}} \quad \text{--- (1)}$$

From above

$$I_s = \frac{V_t}{R_{sh}} + I_t$$



$$I_t = I_s - \frac{V_t}{R_{sh}} \quad \text{--- (2)}$$

From above eq ① & eq ② when $R_{se} = R_{sh}$ then S.T is possible

As... ~~also~~ voltage source V_s and internal resistance R_{se} can be replaced by equivalent current source I_s in parallel with shunt resistance i.e $I_s = \frac{V_s}{R_s}$ & $R_{sh} = R_s$.


Prob!-

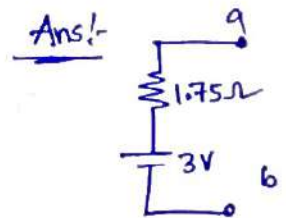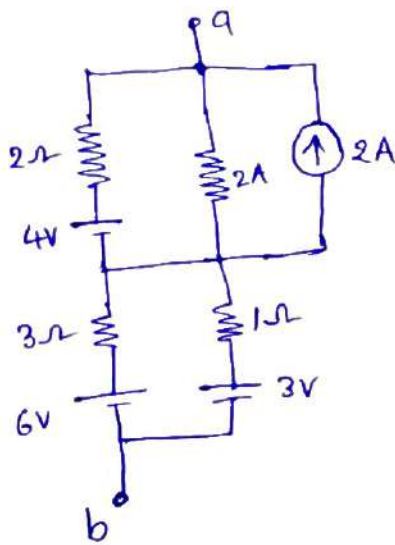Convert given circuit into single voltage source.



Current Division in parallel circuit

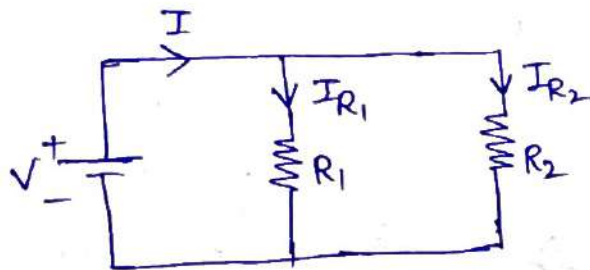For a given circuit current division applied as



i.e $\text{Current in branch} = \text{Total Current} \times \frac{\text{opposite Resistance}}{\text{Total Resistance}}$


i.e $\text{Current in } I_{R_1} = I \times \frac{R_2}{R_1 + R_2}$

$I_{R_2} = I \times \frac{R_1}{R_1 + R_2}$

i.e $I_{R_n} = I \cdot \frac{R_1 \cdot R_2 \dots R_{n-1}}{\sum R_1 R_2 \dots R_n}$

Voltage division in series circuits

VDR - is apply for a given circuit

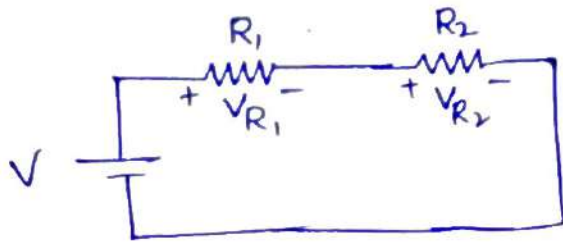

i.e. voltage across any $\frac{\text{branch}}{\text{Resistance}} = \text{Total voltage} \times \frac{\text{Some Resistance}}{\text{Total Resistance}}$


i.e. voltage across R_1 is $\text{Total current} \times \text{Some Resistance}$

$$V_{R_1} = V \times \frac{R_1}{R_1 + R_2} \quad \text{or} \quad I_T R_1 \quad \text{i.e.} \quad V_{R_n} = V \cdot \frac{\sum R_1, R_2, \dots, R_n}{\sum R_n}$$


$$V_{R_2} = V \times \frac{R_2}{R_1 + R_2} \quad \text{or} \quad I_T R_2$$

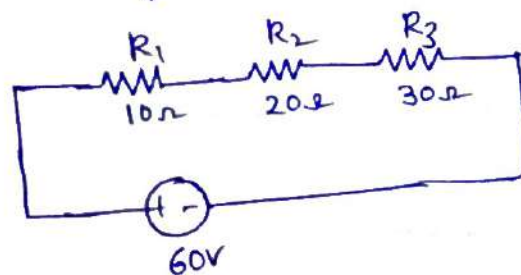Problems:-

①. Find the voltage across 3-resistors by using VDR.



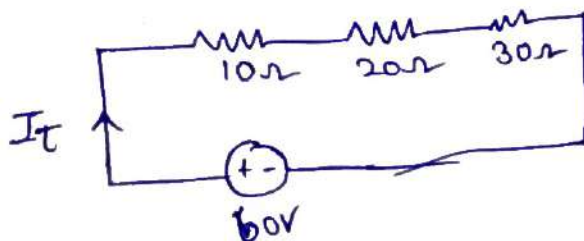Solution:- Let total current I_T & Total voltage $V_t = 60V$




$$R_T = R_1 + R_2 + R_3 \\ = 10 + 20 + 30 = 60\Omega$$

$$I_t = \frac{V_t}{R_t} = \frac{60}{60} = 1A$$

$$V_{10\Omega} = I_T R_{10} = 1 \times 10 = 10V$$

$$V_{20\Omega} = 20 \times 1 = 20V \quad \& \quad V_{30\Omega} = 30V$$

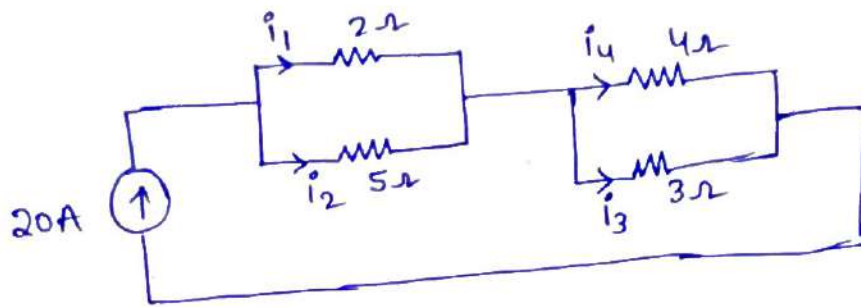Q Find currents i_1 , i_2 , i_3 & i_4 in given circuit.



Solution

In a given circuit total current $I = 20A$, then


$$i_1 = I \times \frac{5}{2+5} = 20 \times \frac{5}{7} = \frac{100}{7} \Rightarrow \boxed{i_1 = 14.28 \text{ Amp}}$$

$$i_2 = 20 \times \frac{2}{2+5} = \frac{40}{7} \Rightarrow \boxed{i_2 = 5.71 \text{ Amp}}$$

$$i_3 = 20 \times \frac{4}{4+3} = \frac{80}{7} = \boxed{i_3 = 11.42 \text{ Amp}}$$

$$i_4 = 20 \times \frac{3}{4+3} = \frac{60}{7} \Rightarrow \boxed{i_4 = 8.57 \text{ Amp}}$$

Prob!- Find the current in all branches

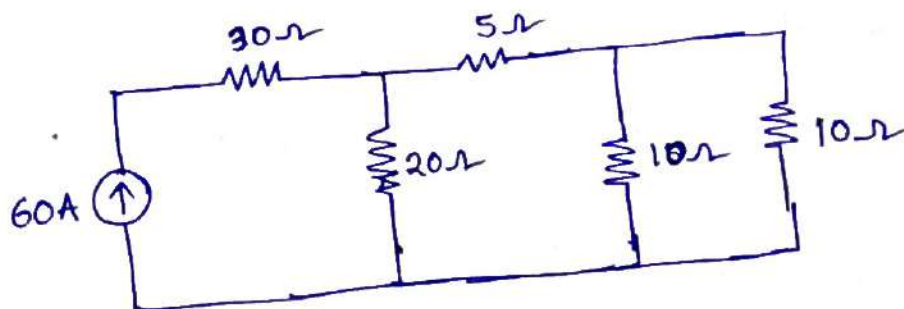

Nodal analysis :-

- This method is mainly based on "Kirchhoff Current Law"
- If a network has 'n' nodes (or) 'j' junction points, then we will get $(n-1)$ (or) $(j-1)$ nodal equations.


Steps for Nodal Analysis :-

- Step ① choose the nodes & node voltages
- Step ②. Assume the ~~one~~ one of the node as "base node (or) reference node" & Assume remaining all ~~are~~ nodes are high potential nodes
- Step ③ Assume the branch currents ^{leaving} ~~leaving~~ from high potential node by using KCL at node
- Step ④ obtain the current (or) nodal equations in terms of node voltages
- Step ⑤ Solving the nodal equations we get node voltages w.r.to them find branch currents.

Note :- If a network has a more no. of voltage sources then better to use mesh analysis otherwise nodal analysis. if network ~~at~~ has $m < n$ then nodal method is preferred.

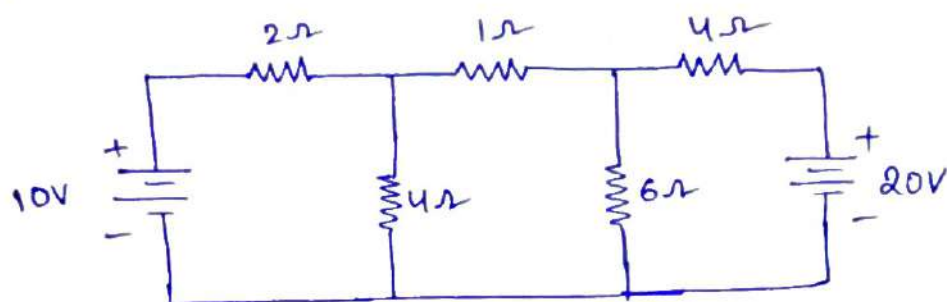problem:-

Find the current through each resistor of circuit shown in figure, by using nodal analysis




Solution:-

→ choose nodes & node voltages, let a one node as reference

→ Assume branch currents as I_1, I_2, I_3 at node ①.

and I_4 & I_5 at node ② as

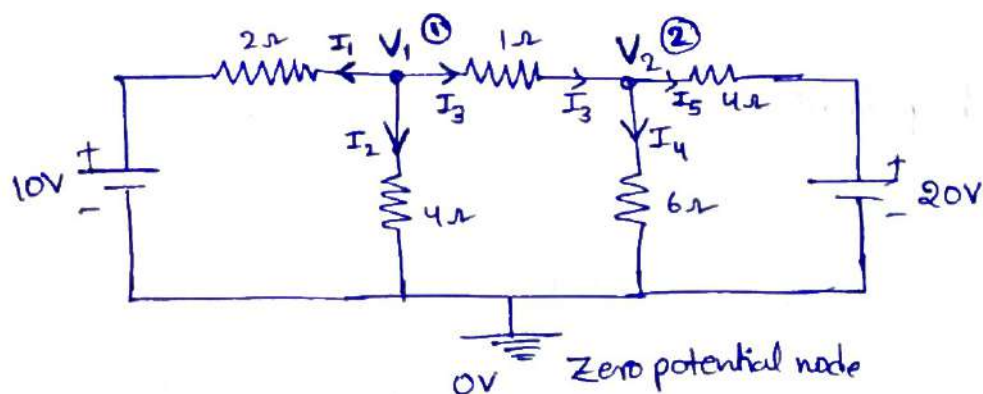

→ At node 1, by applying KCL

$$-I_1 - I_2 - I_3 = 0$$

Now

$$-\left[\frac{V_1 - 10}{2}\right] - \left[\frac{V_1}{4}\right] - \left[\frac{V_1 - V_2}{1}\right] = 0$$

$$-2(V_1 - 10) - V_1 - 4[V_1 - V_2] = 0$$

$$-2V_1 + 20 - V_1 - 4V_1 + 4V_2 = 0$$

$$-7V_1 + 4V_2 = -20 \quad \text{--- (1)}$$

$$\text{We know } I_1 = \frac{V_1 - 10}{2}$$

$$I_2 = \frac{V_1 - 0V}{4} = \frac{V_1}{4}$$

$$I_3 = \frac{V_1 - V_2}{1}$$

→ At node-2 :

$$I_3 - I_4 - I_5 = 0$$

$$I_4 = \frac{V_2}{6}$$

$$I_5 = \frac{V_2 - 20}{4}$$

$$\frac{V_1 - V_2}{1} - \frac{V_2}{6} - \frac{V_2 - 20}{4} = 0$$

$$12(V_1 - V_2) - 2V_2 - 3(V_2 - 20) = 0$$

$$12V_1 - 17V_2 = -60 \quad \text{--- (2)}$$

By solving eq (1) & eq (2).

$$V_1 = 8.169V \quad \& \quad V_2 = 9.295V$$

Now branch currents $I_1 = \frac{V_1 - 10}{2} = \frac{8.169 - 10}{2} = -0.9155$

i.e. $I_1 = 0.9155 \text{ Amp} \rightarrow$ ~~-~~ -ve means opposite direction


$$I_2 = \frac{V_1}{4} = \frac{8.169}{4} = 2.042 \Rightarrow I_2 = 2.042 \text{ A}$$

$$I_3 = \frac{V_1 - V_2}{1} = 1.126 \Rightarrow I_3 = 1.126 \text{ A}$$

$$I_4 = \frac{V_2}{6} = 1.361 \Rightarrow I_4 = 1.361 \text{ A}$$

$$I_5 = \frac{V_2 - 20}{4} = -2.676 \Rightarrow I_5 = 2.676 \text{ A} \leftarrow$$

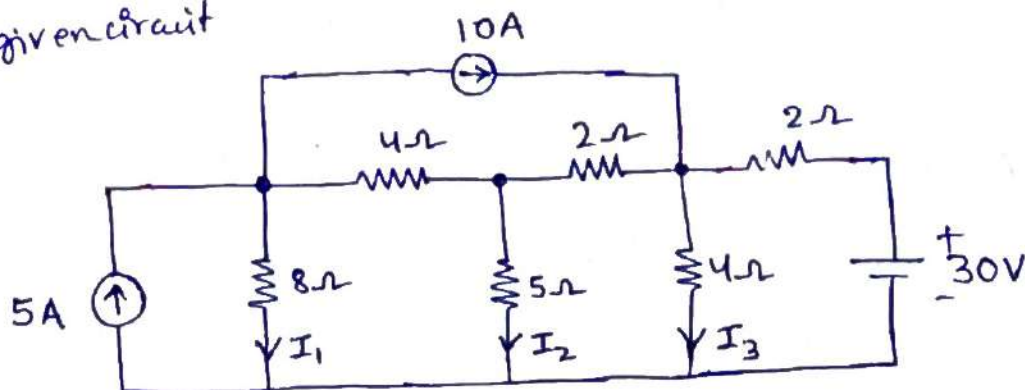Problem:- Find the different node voltages & currents $I_1, I_2, \& I_3$ for given circuit



Mesh analysis (or) Loop Analysis

→ This method is mainly based on KVL

→ If a network have 'b' of branches, 'J' of junctions, then we will get the independent mesh equations

$$\text{i.e } m = b - (J - 1) \quad \text{or} \quad b - (n - 1)$$

Steps for mesh analysis :-


Step ①. Find the various loops in a network.

②. Indicate the assumed loop currents directions and w.r.to that mark the polarities

Note! Assumed loop current is higher value compare with other loop currents.

Step ③ choose minimum no. of loops and write the loop equations by applying KVL

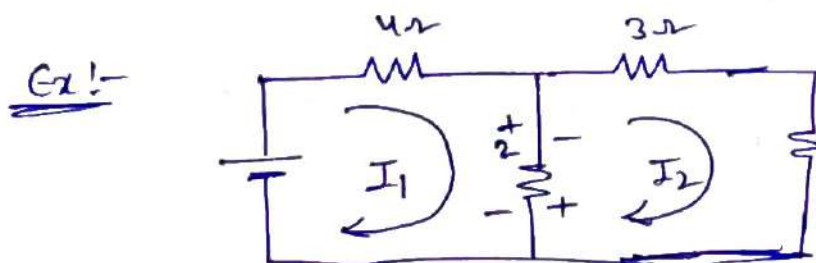Step ④ By Solving the loop equations we get loop currents.



At Loop-1


$$\text{Voltage At } 2\Omega \quad V_{2\Omega} = 2(I_1 - I_2)$$

At Loop-2

$$V_{2\Omega} = 2(I_2 - I_1)$$

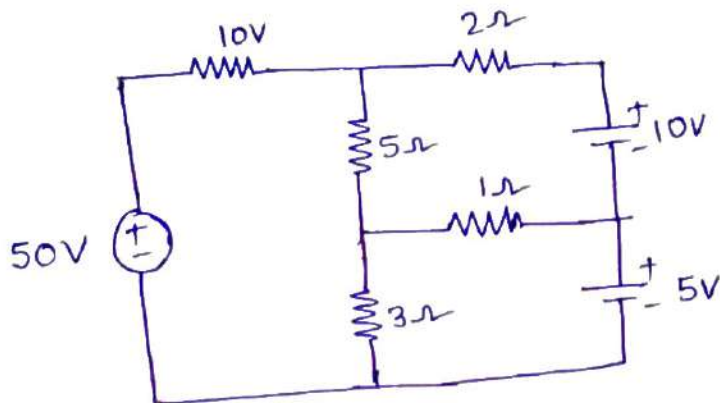
Problem:-

① Determine mesh current by using mesh analysis



Solution:-

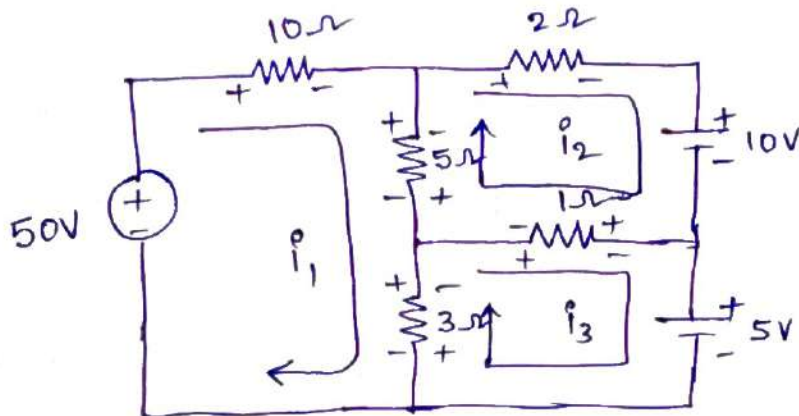step ① Assuming loop currents i_1 , i_2 & i_3



step ② At loop-1, Apply KVL

$$50 - 10i_1 - 5(i_1 - i_2) - 3(i_1 - i_3) = 0$$

$$-18i_1 + 5i_2 + 3i_3 + 50 = 0$$

$$-18i_1 + 5i_2 + 3i_3 = -50 \quad \text{--- ①}$$

At loop-2,

$$-2i_2 - 10 - 1(i_2 - i_3) - 5(i_2 - i_1) = 0$$

$$5i_1 - 8i_2 + i_3 = 10 \quad \text{--- ②}$$

At loop ③

$$-(i_3 - i_2) - 5 - 3(i_3 - i_1) = 0$$

$$3i_1 + i_2 - 4i_3 = 5 \quad \text{--- ③}$$

by solving eq'n

$$i_1 = 3.300 \text{ Amp} \quad i_2 = 0.997 \text{ A} \quad \& \quad i_3 = 1.474 \text{ A}$$

Current in 10Ω $I_{10\Omega} = 3.3 \text{ A}$

$$I_{5\Omega} = \cancel{(-3.3/4/1/3 + 0.997)} (i_1 - i_2) \\ = 3.3 - 0.997 = 2.303 \text{ A}$$


$$I_{2\Omega} = 0.997 \text{ A}$$

$$I_{1\Omega} = (i_2 - i_3) = 0.997 - 1.474 = -0.477 \text{ A}$$

$$I_{3\Omega} = (i_3 - i_1) = 1.474 - 3.3 = -1.825 \text{ A}$$

Prob ②

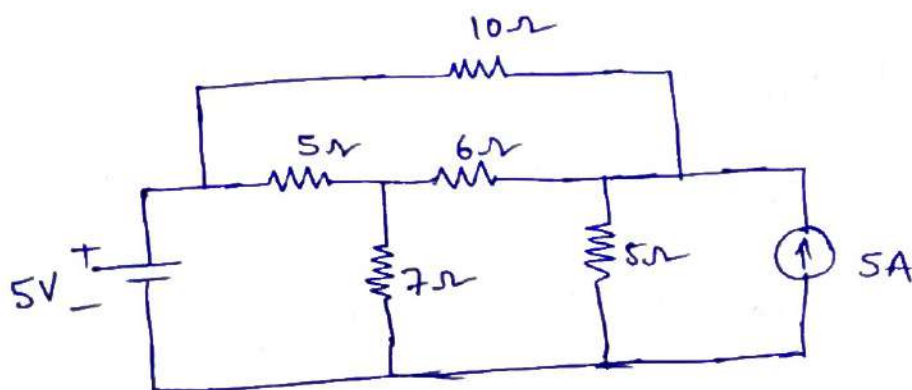Find the voltage across 10Ω resistor in the network




Ans: 9.138V

Star to Delta $\leftrightarrow$ Delta to Star Transformation

Star connection (Y)

If 3-resistors are connected in such a manner that one end of each resistor are connected at a junction point $\leftrightarrow$ star point, then thus 3-resistors are said to be in "star connection"


Ex:-

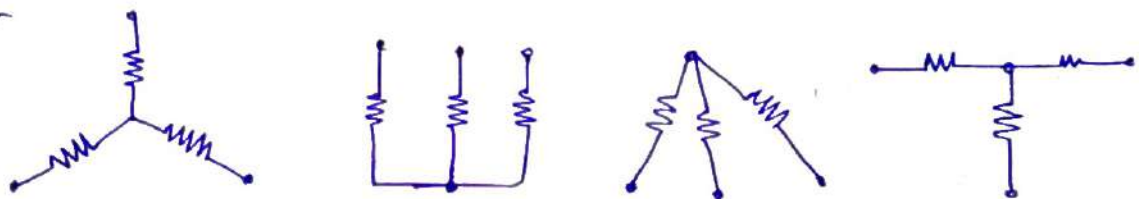

Delta Connection (Δ)

In 3-resistors, one end of the first resistor is connected to the first end of second, the second end of second to first end of third and so on to complete a loop then thus resistors are said to be connected in "Delta"


Ex:-

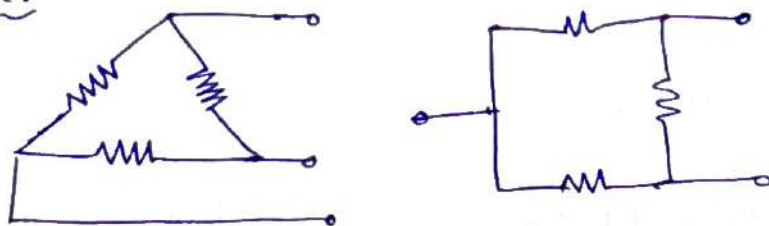

→ These Y & Δ connections are used in 3-phase systems $\leftrightarrow$ machines.

→ These connection can increase the voltages $\leftrightarrow$ current in 3- ϕ systems

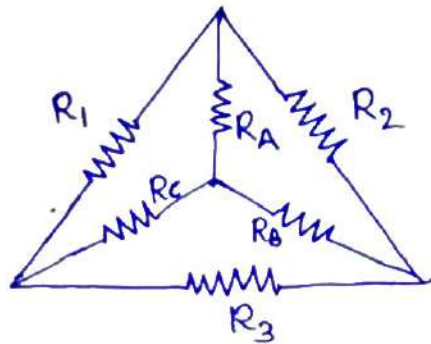Star-to-Delta ($Y \rightarrow \Delta$) Transformation



~~Y~~ $\Delta \rightarrow Y$

Star Resistance values as

$$R_A = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

$$R_B = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$

$$R_C = \frac{R_3 R_1}{R_1 + R_2 + R_3}$$

if $R_1 = R_2 = R_3 = R$ are same

then

$$R_Y = \frac{R_\Delta}{3}$$

~~Y~~ $Y \rightarrow \Delta$

Delta Resistance values as

$$R_1 = \frac{R_A R_B + R_B R_C + R_C R_A}{R_B}$$

$$R_2 = \frac{R_A R_B + R_B R_C + R_C R_A}{R_C}$$

$$R_3 = \frac{R_A R_B + R_B R_C + R_C R_A}{R_A}$$


If $R_A = R_B = R_C = R$

then

$$R_\Delta = 3 R_Y$$

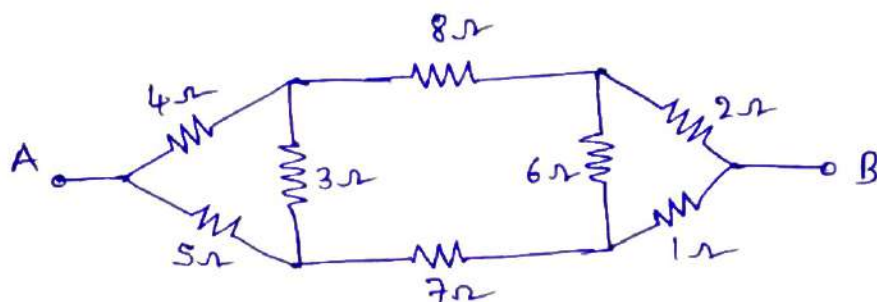
problem:-

P①. Find the voltage to be applied across A-B, if drive current of 20A




Solution:- In a given circuit Δ -2-4 connections are present

As

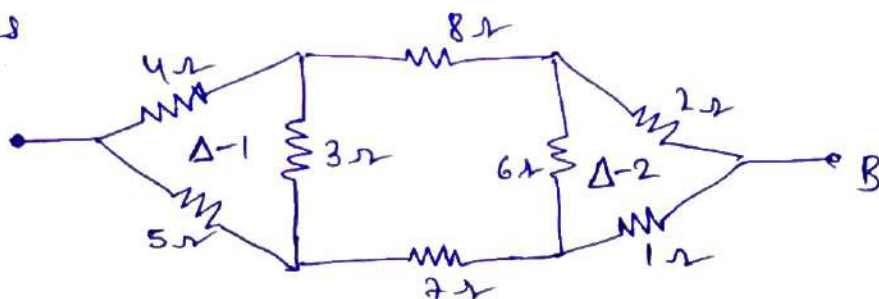


Δ-1

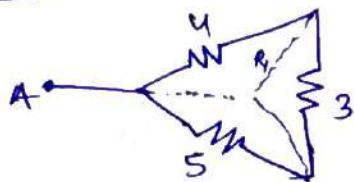

$$R_1 = \frac{4 \times 3}{4 + 3 + 5} = \frac{12}{12} = 1\Omega$$

$$R_2 = \frac{3 \times 5}{3 + 5 + 4} = \frac{15}{12} = 1.25\Omega$$
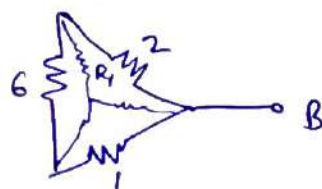
$$R_3 = \frac{5 \times 4}{12} = 1.66\Omega$$






$$R_1 = \frac{6 \times 2}{6 + 2 + 1} = \frac{12}{9} = 1.33\Omega$$

$$R_2 = \frac{2}{9} = 0.22\Omega$$

$$R_3 = \frac{6}{9} = 0.66\Omega$$

Circuit Redrawn as

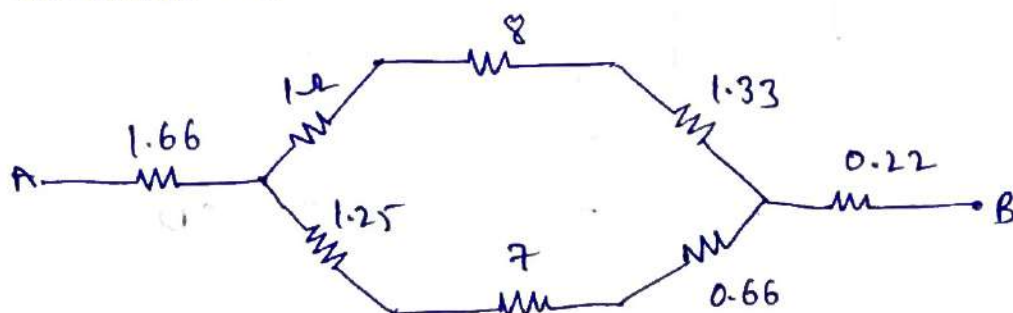

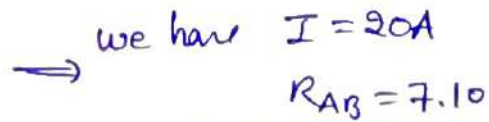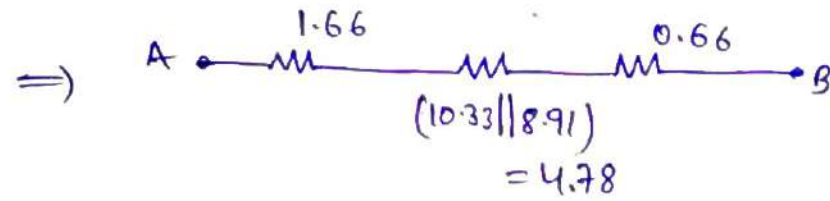

Network Theorems

The necessity of network theorems is to calculate single branch response in complicated network.

- ① Superposition theorem
- ② Thevenin's theorem
- ③ Norton's theorem
- ④ Maximum Power Transfer theorem
- ⑤ Reciprocity theorem


① Superposition Theorem

Statement : In any linear, bilateral network consist of two (or) more sources & Resistors, the response (i.e. V or I) at any element in network is equal to the algebraic sum of the responses caused by individual sources acting separately, while other sources are replaced by their internal resistances at ideal conditions

i.e. Voltage source as $\rightarrow$ short circuit


Current source as $\rightarrow$ open circuit

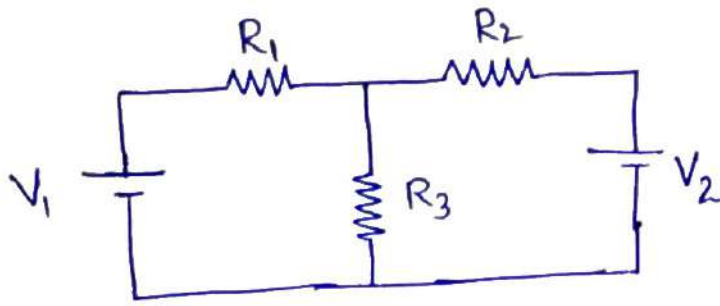Explanation :- consider a dc-circuit which is having two voltage sources V_1 & V_2 , and having 3-resistors R_1, R_2 & R_3 as shown below circuit.



for above circuit verify superposition theorem, take response at " R_3 " - element.

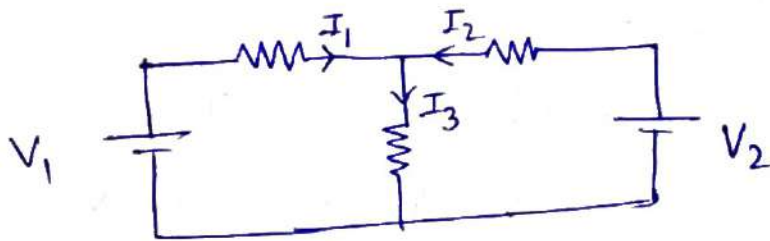
step ① Let all sources as two sources are in Active Condition as i.e. V_1 & V_2 are in ON, then let respective currents as I_1 , I_2 & I_3



$$I_3 = I_1 + I_2$$

where ' I_3 ' is response at ' R_3 ' Resistor

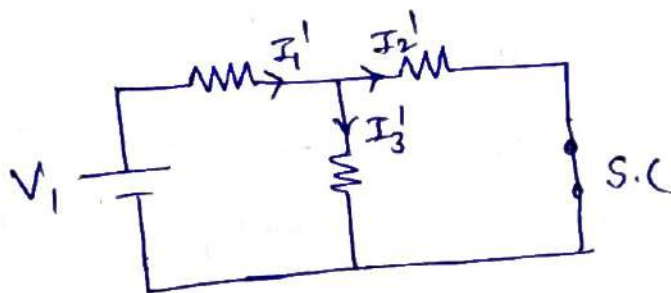
step ② ~~Let~~ Assume the $V_1 = \text{ON}$ & $V_2 = \text{off}$ state then



V_2 is replaced by short circuit

$$I_3' = I_1' - I_2'$$

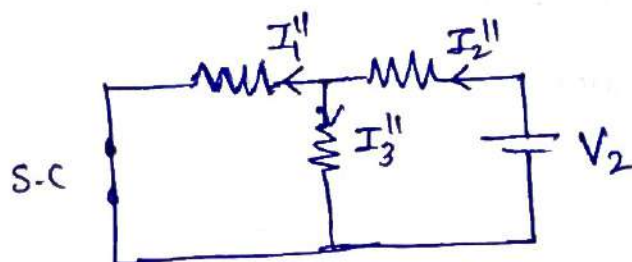step ③ Assume the $V_1 = \text{off}$ & $V_2 = \text{ON}$ state



$$I_3'' = I_1'' + I_2''$$


According to Superposition theorem

$$I_3 = I_3' + I_3''$$

Similarly $I_1 = I_1' + I_1''$ & $I_2 = I_2' + I_2''$

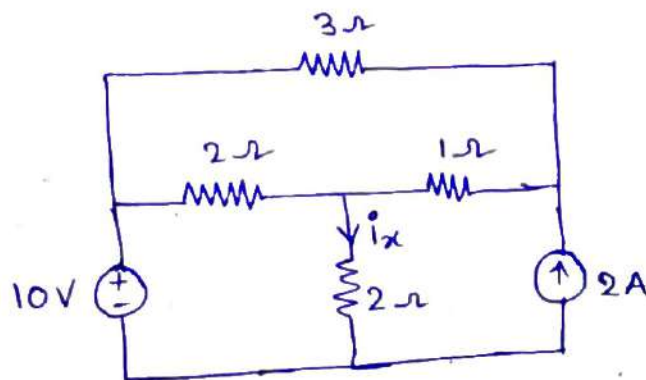Problem :-


Find ' i_x ' for a given circuit using Superposition Theorem.




Solution:- In a given circuit we have 2-sources
 as 10V $\rightarrow$ voltage source
 & 2A $\rightarrow$ current source

Let individual sources acting separately, then

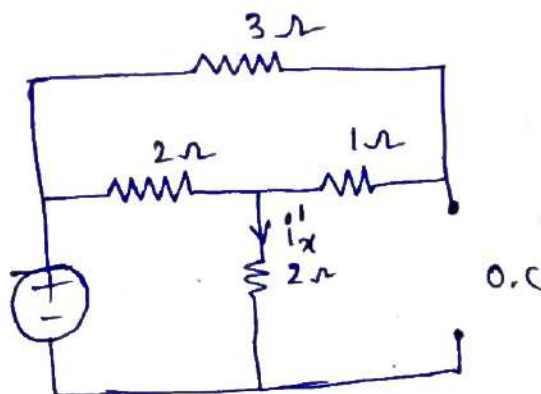
Step ① 10V $\rightarrow$ ON & 2A $\rightarrow$ off, circuit drawn as



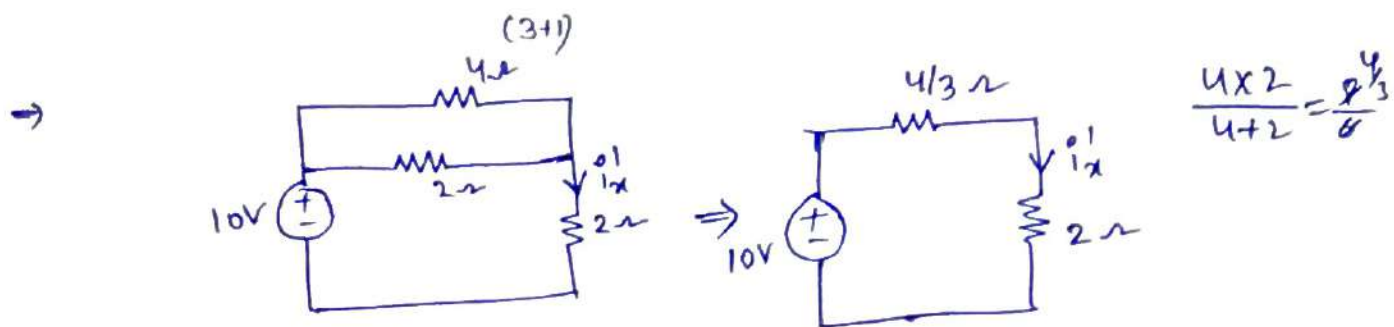

Now $i_x^1 = \frac{10}{\frac{4}{3} + 2} = \frac{10}{10/3} = \frac{30}{10} \Rightarrow \boxed{i_x^1 = 3A}$

Step 2 Let 10V → OFF & 2A → ON, then

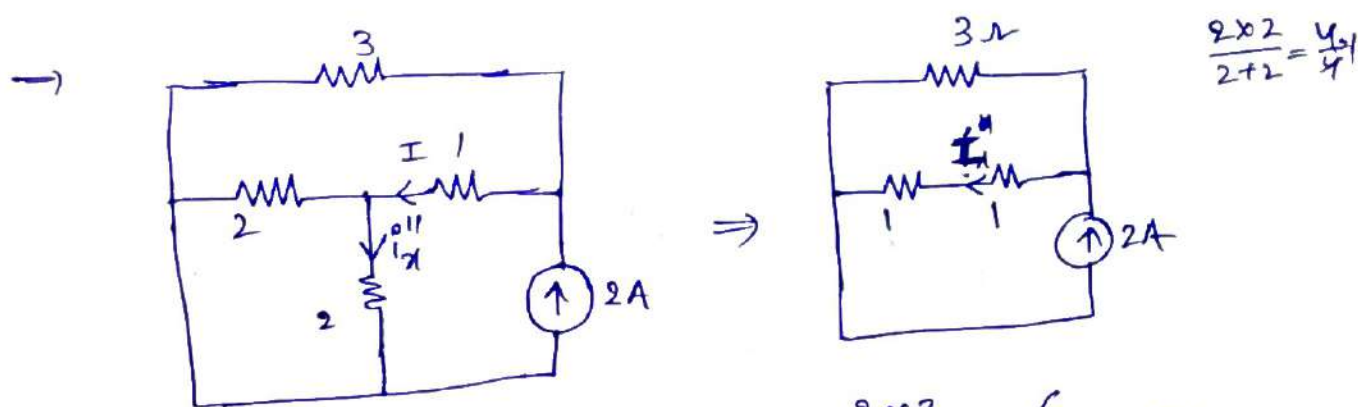

$$I = \frac{2 \times 3}{2 + 3} = \frac{6}{5} = 1.2A$$


$$i_x^2 = I \times \frac{2}{2 + 2} = 1.2 \times \frac{2}{2 + 2} = 0.6A$$

According to superposition theorem

$$i_x = i_x^1 + i_x^2 \Rightarrow i_x = 3 + 0.6 \Rightarrow \boxed{i_x = 3.6A}$$

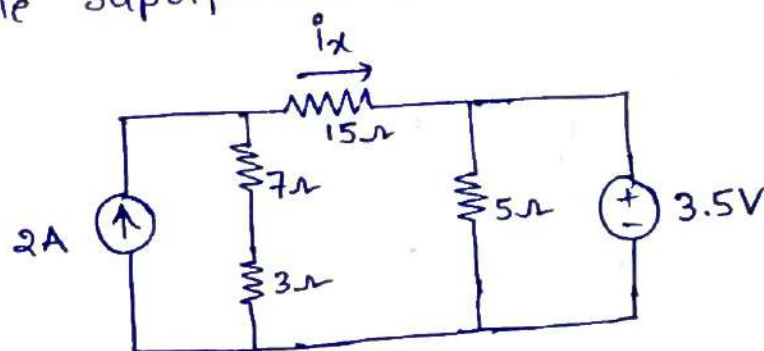Problem:-

Using the superposition theorem compute the current " i_x "




Ans: 660mA.

Thevenin's Theorem :

In any linear, bilateral network consist of more no. of sources and resistors can be replaced by an equivalent circuit of single voltage source in series with Resistor, while ^{all} other sources are replaced by their internal resistances at ideal conditions as


voltage source as short circuit (S.C)

Current source as open circuit

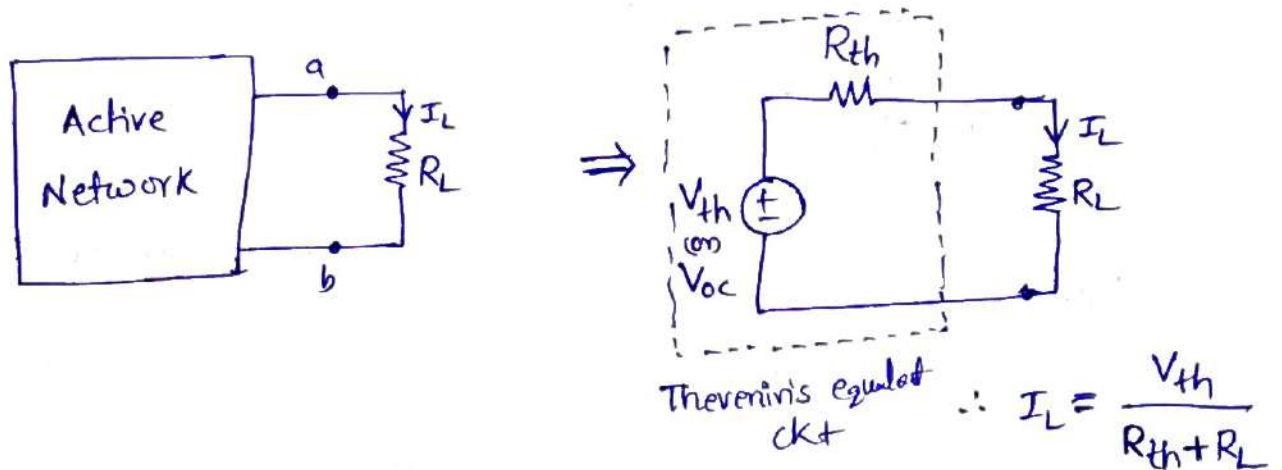

Explanation :- Consider a dc-circuit which is

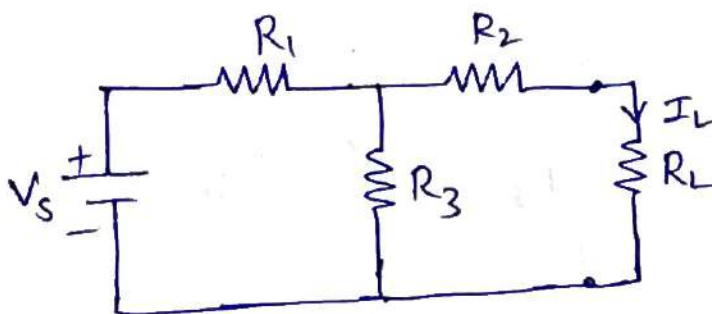having voltage source (V_s), & resistors R_1 , R_2 & R_3 are connected with a load Resistor ' R_L ' as shown below




~~Step~~ Find current in load ' R_L ' using thevenin's theorem

Step 1.. To find ' I_L ' value, we have to find thevenin's equivalent circuit. To find equivalent circuit we have to find " V_{th} & R_{th} "

Step 1 To find ' V_{th} ', remove the load resistor ' R_L ' from the circuit, across open terminal find the voltage ($V_{o.c}$)


Then circuit modified as

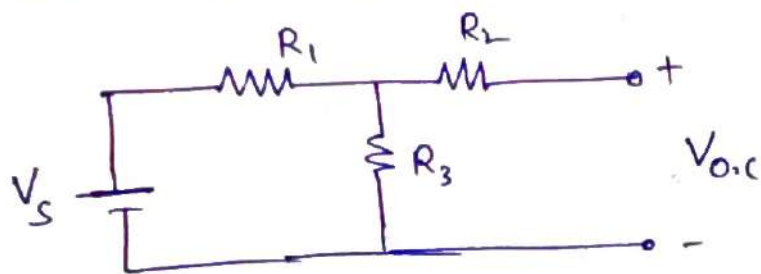

Let $I \rightarrow$ current flows in circuit, $R_2 = 0$ because no current flows, then $V_{o.c} =$ voltage across R_3 resistor


$$V_{oc} = I R_3$$

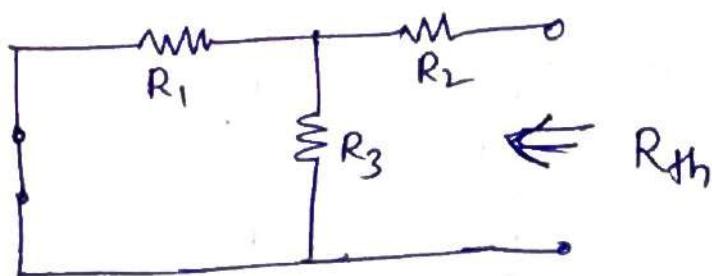Step 2 To find ' R_{th} ', voltage source is replaced by its internal resistance, as



then
$$R_{th} = R_2 + (R_1 \parallel R_3)$$

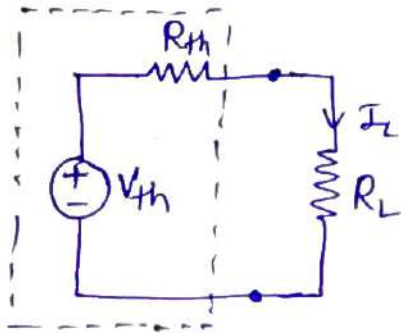
Step 3 The thevenins equivalent circuit drawn as



$$I_L = \frac{V_{th}}{R_{th} + R_L}$$


$$P_L = I_L^2 R_L$$

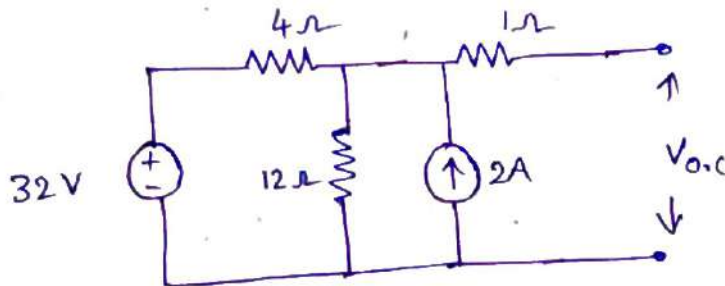Problem 1: Find current flowing in load resistor ' $R_L = 10\Omega$ ' using thevenin's theorem for a given circuit



Solution:

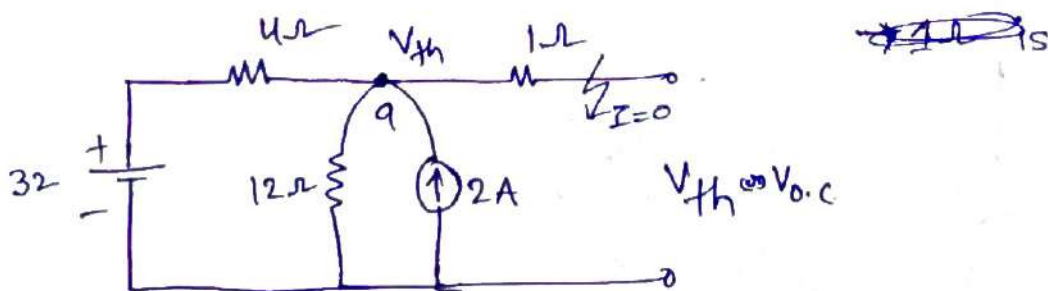Step 1: To find " $V_{oc} = V_{th}$ ", circuit redrawn as




→ In 1Ω resistor $I_o = 0$, at node 'a' V_{th} will appear, then by using nodal analysis

$$\frac{V_{th} - 32}{4} + \frac{V_{th}}{12} - 2 = 0$$

$$\Rightarrow 3V_{th} - 96 + V_{th} - 24 = 0$$

$$V_{th} = \frac{120}{4} = \boxed{V_{th} = 30V}$$

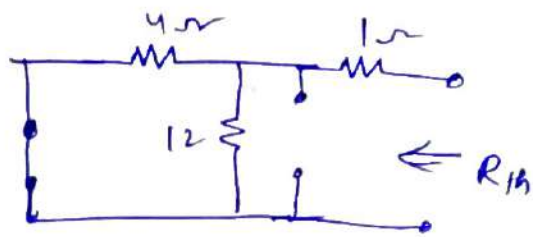
Step ②:- To find ' R_{th} ' all sources are replaced by their resistance



$$R_{th} = 1 + \frac{4 \times 12}{4 + 12}$$

$$= 1 + 3 = 4 \Omega$$

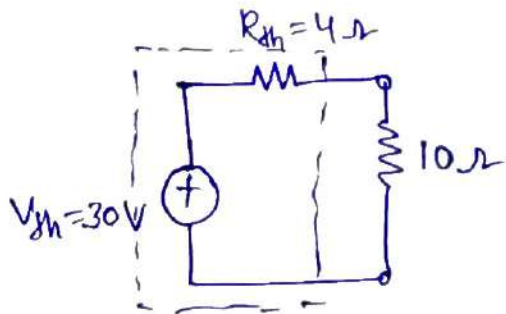
Current flowing through load resistor can be found by thevenin's equivalent circuit as



$$I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{30}{4 + 10} = \frac{30}{14} = 2.142 \text{ Amp}$$

$$I_L = 2.142 \text{ Amp}$$

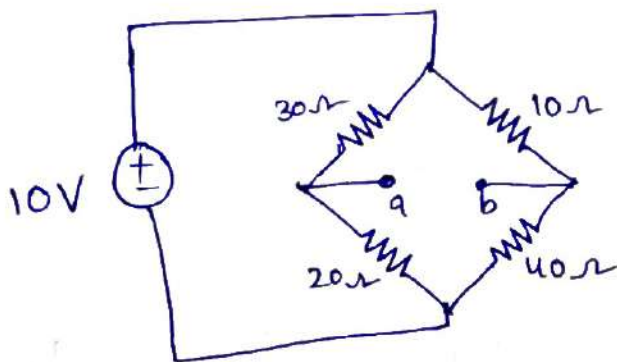Prob ②:- Find thevenin's equivalent circuit for a given circuit




Ans:- $V_{th} = -4V$
 $R_{th} = 20 \Omega$

Norton's Theorem

In any linear, bilateral network consist of more no. of sources and resistors can be replaced by an equivalent circuit of single current source in parallel with resistor, while all other sources are replaced by their internal resistances at ideal conditions as


Voltage source as short circuit (S.C)

Voltage source as open circuit (O.C).

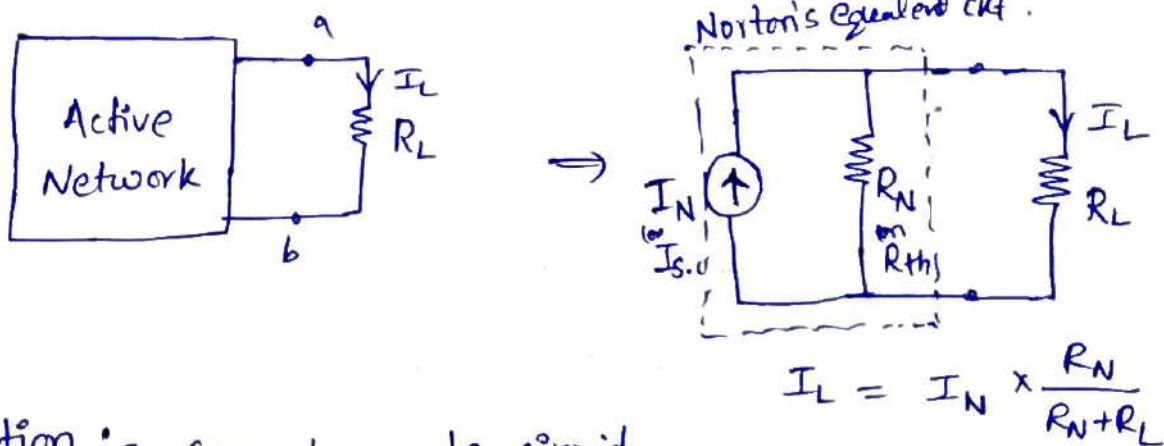

Explanation :- Consider a dc-circuit

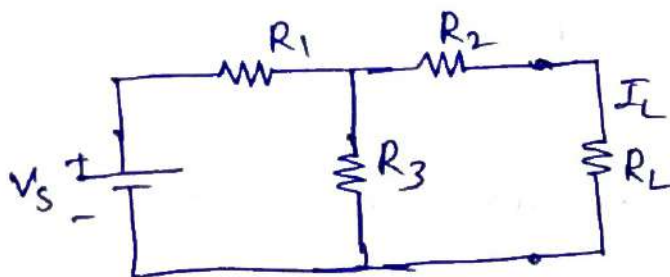
which is having voltage source (V_S), resistors R_1 , R_2 & R_3 are connected with load resistor ' R_L ' as shown below



To find Norton's equivalent circuit, we have to find


I_N & R_N

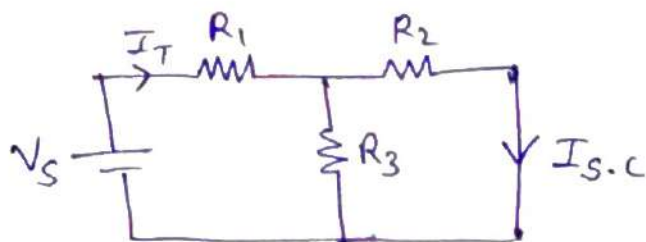Step ① To find " I_N " remove the ' R_L ' and short circuit the terminals, as norton's current I_N ($\propto I_{s.c}$), then




Here $I_{s.c}$ is current flowing R_2 i.e. $I_{s.c} = I_T \times \frac{R_3}{R_2 + R_3}$
 $I_T = \text{Total current}.$

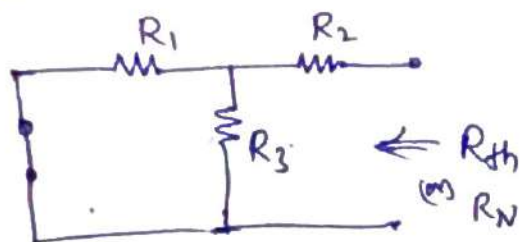Step ② To find R_N ($\propto R_{th}$), voltage source is replaced by its internal resistance as



$$\Rightarrow R_N = R_2 + (R_1 \parallel R_3)$$

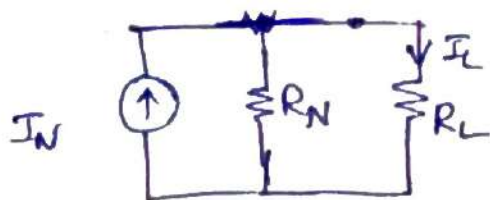Step ③ The Norton's equivalent circuit as




$$I_L = I_N \times \frac{R_N}{R_N + R_L}$$

$$P_L = I_L^2 R_L.$$


Prob:-

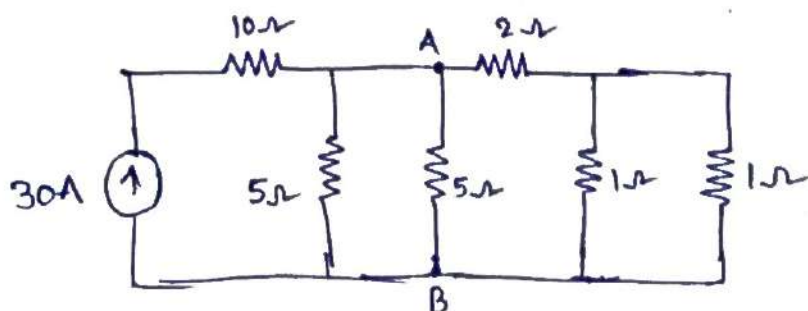① Determine the current through AB in the network.




Solution:- In given circuit AB is 5Ω resistor is load Resistor $R_L = 5\Omega$

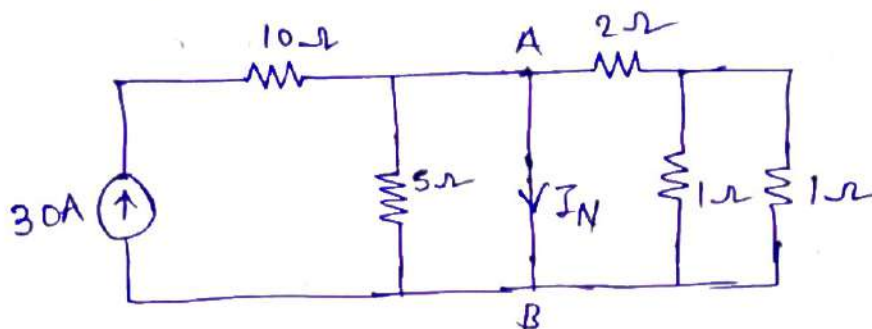step ① To find I_N ; the AB ~~branch~~ is short circuited, then circuit redrawn as




When AB-branch circuited, then all currents passes through AB branch, then no-current in 2Ω , 1Ω 's & 5Ω resistor

As

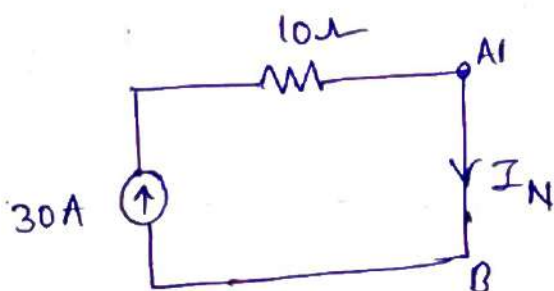


$$\text{since } I_N = 30\text{A}$$

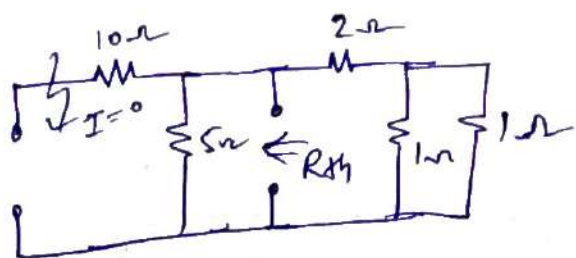step ② To find R_N , AB branch is removed then



$$\begin{aligned} \text{So } I_N &= \{(1 \parallel 1) + 2\} \parallel 5 \\ &= \frac{2.5 \times 5}{2.5 + 5} = 1.67\Omega \end{aligned}$$

step ③ Norton equivalent circuit

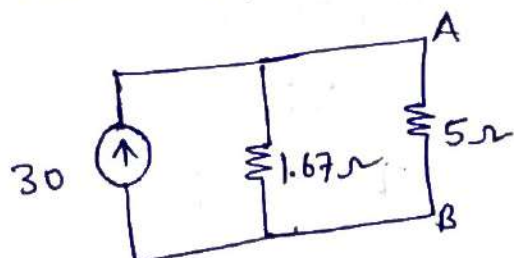

$$\Rightarrow I_L = 30 \times \frac{1.67}{1.67 + 5}$$

$$\boxed{I_L = 7.5\text{A}}$$


Time-domain analysis of first order RL & RC circuits

Time domain analysis (or) Time response analysis is ~~one~~ nothing that the responses of circuits analysed in time domain.

Time Response Analysis of First order RL-circuit

Consider a series RL circuit as shown in figure below, which is excited by a DC-Source $V_i(t)u(t)$

Applying KVL to the
for given circuit

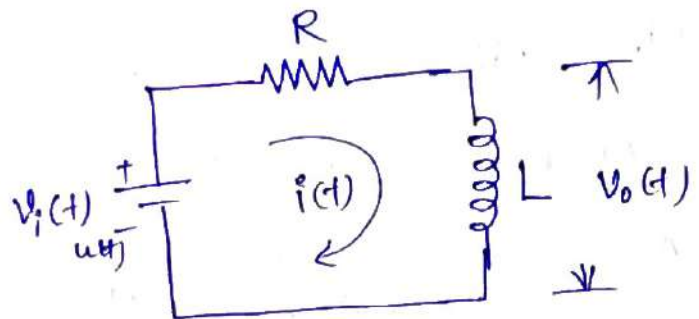

$$L \frac{di(t)}{dt} + Ri(t) = V_i(t)u(t)$$

Taking Laplace transform on both sides of the equation

$$L \{sI(s) - i(0)\} + RI(s) = \frac{V_i}{s}$$

Initial $i(0) = 0$, then

$$LSI(s) + RI(s) = \frac{V_i}{sL}$$

$$I(s) = \frac{V_i}{sL \left[s + \frac{R}{L} \right]}$$

$$\Rightarrow I(s) \left[Ls + R \right] = \frac{V_i}{s}$$

$$I(s) = \frac{V_i}{s \left[Ls + R \right]}$$

$$I(s) = \frac{V_i}{sL \left[s + \frac{R}{L} \right]}$$

Using partial fraction for above equation

$$I(s) = \frac{A_1}{s} + \frac{A_2}{s + \frac{R}{L}}$$

where $A_1 = s I(s) \Big|_{s=0} = \frac{V_i}{L} \times \frac{1}{s + \frac{R}{L}} \Big|_{s=0} \Rightarrow A_1 = \frac{V_i}{R}$

$$A_2 = \left(s + \frac{R}{L}\right) I(s) \Big|_{s = -\frac{R}{L}} = \frac{V_i}{L} \times \frac{1}{s} \Big|_{s = -\frac{R}{L}} = A_2 = -\frac{V_i}{R}$$

Therefore $I(s) = \frac{V_i/R}{s} + \frac{-\frac{V_i}{R}}{s + \frac{R}{L}}$

$$I(s) = \frac{V_i}{R} \left[\frac{1}{s} - \frac{1}{s + \frac{R}{L}} \right]$$

Taking inverse Laplace transform, we get


$$i(t) = \frac{V_i}{R} \left[1 - e^{-\frac{R}{L}t} \right]$$

By this equation time ~~equation~~ response of system is

For RL-circuit

Time constant value is


$$\tau = \frac{R}{L} \text{ seconds}$$

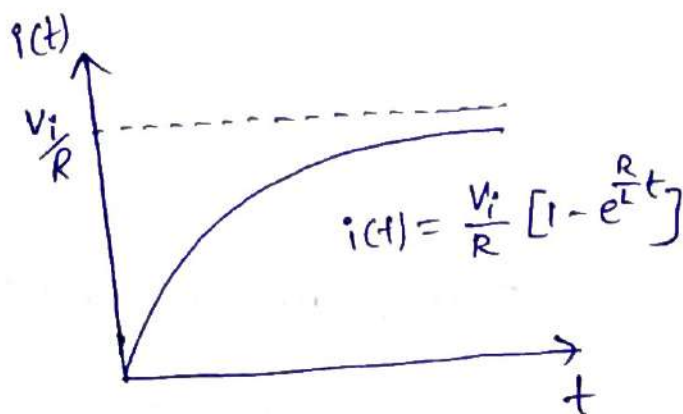

Time Response Analysis of First Order RC-Circuit

consider a series RC-circuit as shown figure, excited by DC-source $V_i u(t)$.

using KVL to the circuit

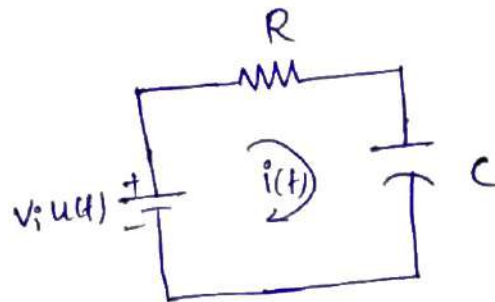

$$\frac{1}{C} \int_{-\infty}^t i(t) dt + R i(t) = V_i u(t)$$

$$\text{i.e. } R i(t) + \frac{1}{C} \int_{-\infty}^0 i(t) dt + \frac{1}{C} \int_0^t i(t) dt = V_i u(t)$$

Taking Laplace transform on both sides.

$$R I(s) + \frac{1}{C} \left[\frac{I(s)}{s} + \frac{q(0^+)}{s} \right] = \frac{V_i}{s}$$

$\therefore q(0^+) = 0$
C is uncharged

Therefore $R I(s) + \frac{1}{Cs} I(s) = \frac{V_i}{s}$

$$I(s) \cdot \left[R + \frac{1}{Cs} \right] = \frac{V_i}{s}$$

$$I(s) = \frac{\frac{V_i}{s}}{R + \frac{1}{Cs}} \Rightarrow I(s) = \frac{V_i/s}{R/s \left[s + \frac{1}{RC} \right]}$$

$$I(s) = \frac{V_i}{R \left[s + \frac{1}{RC} \right]}$$


Taking inverse Laplace Transform

$$i(t) = \frac{V_i}{R} e^{-\frac{t}{RC}}$$

The time response of the first order series RC circuit is

Time constant

$$\tau = \frac{1}{RC} \text{ sec.}$$

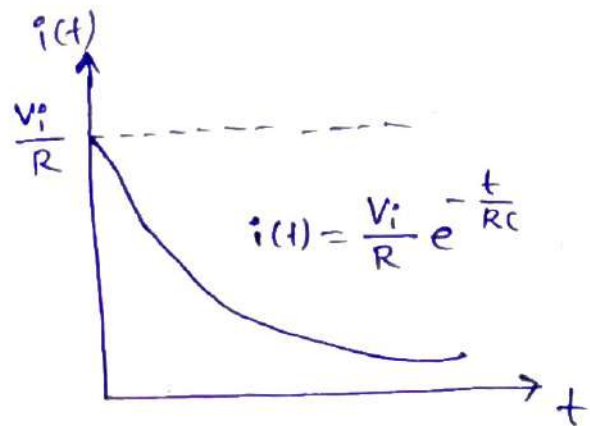


Problem:-

Derive the expression for the current in the circuit as shown in figure

Solution:-

Applying KVL to the given

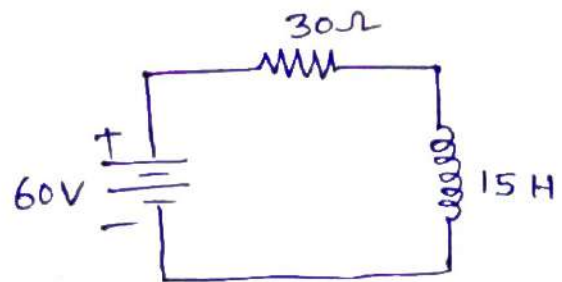

$$15 \frac{di(t)}{dt} + 30i(t) = 60$$

$$\frac{di(t)}{dt} + 2i(t) = 4$$

Taking Laplace transform on both sides, we get

$$\{sI(s) - i(0^-)\} + 2I(s) = \frac{4}{s}$$

Since $i(0^-) = 0$, we get

$$I(s) = \frac{4}{s(s+2)}$$

using partial fraction

$$I(s) = \frac{4}{s(s+2)} = \frac{A_1}{s} + \frac{A_2}{s+2}$$

where $A_1 = s I(s) \Big|_{s=0} = \frac{4}{s+2} \Big|_{s=0} = 2$

$$A_2 = (s+2) I(s) \Big|_{s=-2} = \frac{4}{s} \Big|_{s=-2} = -2$$

Therefore $I(s) = \frac{2}{s} - \frac{2}{s+2}$

Taking Inverse Laplace transform, we get

$$i(t) = 2 (1 - e^{-2t}) A$$

 x